

1.

$$U = 400 \text{ V} ; f = 50 \text{ Hz}$$

Belastung I: Y-koppl.; $R = 20$; $C = 100 \mu\text{F}$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi \cdot 50 \cdot 100 \cdot 10^{-6}} = 31,83 \Omega/\text{phas}$$


$$Z_1 = (20 - j31,83) \Omega/\text{phas}$$

Belastung II: Δ -koppl.; $L = 100 \text{ mH}$

$$X_L = \omega L = 2\pi \cdot 50 \cdot 100 \cdot 10^{-3} = 31,42 \Omega$$

$$Z_\Delta = j31,42$$

Ekv. Y-fas:

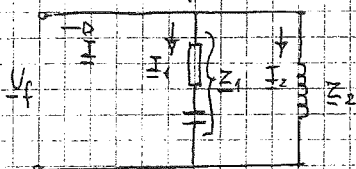

$$Z_2 = \frac{Z_\Delta}{3} = j10,47 \Omega/\text{phas}$$

$$a) \quad \underline{I}_1 = \frac{U_f}{Z_1} = \frac{\frac{400}{\sqrt{3}} \angle 0^\circ}{20 - j31,83} = \frac{\frac{400}{\sqrt{3}} \angle 0^\circ}{37,59 \angle -57,86^\circ} = \underline{\underline{6,14 \angle 57,86^\circ = (3,27 + j5,2) \text{ A}}}$$

$$\underline{I}_2 = \frac{U_f}{Z_2} = \frac{\frac{400}{\sqrt{3}} \angle 0^\circ}{j10,47} = \underline{\underline{22,05 \angle -90^\circ \text{ A}}}$$

$$\underline{I} = \underline{I}_1 + \underline{I}_2 = 3,27 + j5,2 - j22,05 = 3,27 - j16,85 = \underline{\underline{17,16 \angle -79^\circ \text{ A}}}$$


$$|\underline{I}_A| = \frac{|\underline{I}|}{\sqrt{3}} \Rightarrow |\underline{I}_A| = \underline{\underline{12,73 \text{ A}}}$$

c) Belastung I - kap. charakter

Belastung II - ind. charakter

Totallasten - ind. charakter
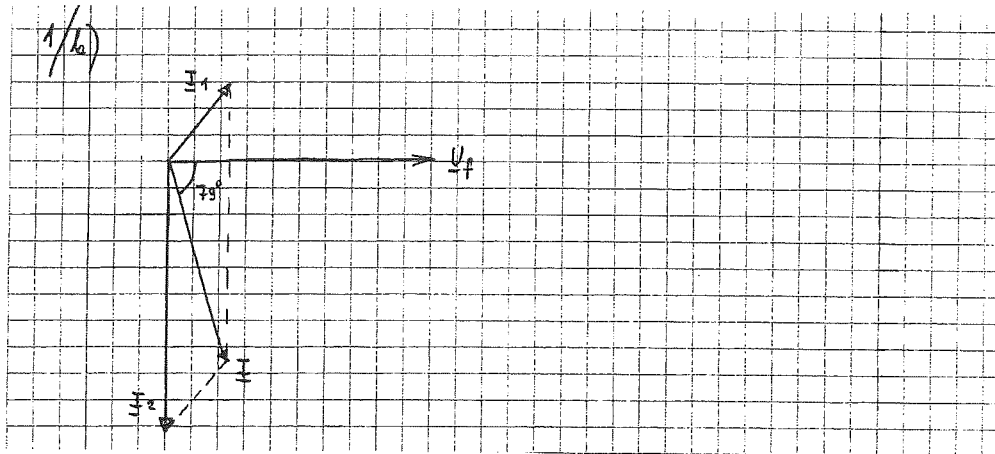
$$d) \quad S = 3 U_f \underline{I}^* = 3 \cdot \frac{400}{\sqrt{3}} \angle 0^\circ \cdot 17,16 \angle 79^\circ = 11,89 \cdot 10^3 \angle 79^\circ = \underline{\underline{(2269 + j11672) \text{ VA}}}$$



2 a)

1. Före inkoppling av AM och C:

$$U = 400 \text{ V}; f = 50 \text{ Hz}; P_i = 140 \text{ kW}; \cos \varphi_i = 0,707$$

$$\Rightarrow Q_i = 140 \text{ kVAR} \Rightarrow S_i = \sqrt{P_i^2 + Q_i^2} = \sqrt{2} \cdot 140 \text{ kVA}$$

$$I = \frac{S_i}{\sqrt{3} \cdot U} = \frac{140 \cdot \sqrt{2} \cdot 10^3}{\sqrt{3} \cdot 400} = \underline{\underline{235,3 \text{ A}}}$$

2. Efter inkoppling av AM och C:

$$Q_c = 3 \omega C U_v^2; U_c = U = 400 \text{ V}; C = 1 \cdot 10^{-3} \text{ F}$$

$$Q_c = 3 \cdot 100 \pi \cdot 1 \cdot 10^{-3} \cdot 400^2 = 150,8 \text{ kVAR}$$

$$P_m = 15 \text{ kW}; I_m = 28,5 \text{ A} \Rightarrow S_m = \sqrt{3} \cdot 400 \cdot 28,5 = 19,75 \text{ kVA}$$

$$Q_m = \sqrt{S_m^2 - P_m^2} = 12,84 \text{ kVAR}$$

Från nätet:

$$P = P_i + P_m = 140 + 15 = 155 \text{ kW}$$

$$Q = Q_i + Q_m - Q_c = 140 + 12,84 - 150,8 = 2,04 \text{ kVAR}$$

$$I = \frac{S}{\sqrt{3} \cdot U} = \frac{\sqrt{155^2 + 2,04^2} \cdot 10^3}{\sqrt{3} \cdot 400} = \underline{\underline{223,7 \text{ A}}}$$

$$\underline{\underline{\cos \varphi}} = \frac{P}{S} = \frac{155}{155,01} \approx \underline{\underline{1}}$$

~~3.~~

3. En 3-fas trafo: $S_n = 100 \text{ kVA}$; $6,6/0,4 \text{ kV}$
 $x_k = 5,5\%$, $r_k = 1,0\%$


a) $I_2 = 125 \text{ A}$; $\cos \varphi_2 = 0,8$; $U_1 = 6,6 \text{ kV}$; $U_2 = ?$

Beräkningar på nedsp sidan:

$$Z_k = x_k Z_{\text{bas}} = 0,055 \cdot \frac{400^2}{100 \cdot 10^3} = 88 \cdot 10^{-3} \Omega/\text{fas}$$

$$R_k = r_k Z_{\text{bas}} = 0,01 \cdot \frac{400^2}{100 \cdot 10^3} = 16 \cdot 10^{-3} \Omega/\text{fas}$$
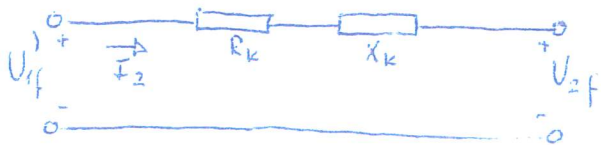
$$X_k = \sqrt{Z_k^2 - R_k^2} = 86,5 \cdot 10^{-3} \Omega/\text{fas}$$



$$U_{1f} = \frac{400}{\sqrt{3}} \text{ V}$$

$$\Delta U = \sqrt{3} I_2 (R_k \cos \varphi_2 + X_k \sin \varphi_2) = \sqrt{3} \cdot 125 (16 \cdot 10^{-3} \cdot 0,8 + 86,5 \cdot 10^{-3} \cdot 0,6) = 14 \text{ V}$$

$$\underline{U_2 = 400 - 14 = 386 \text{ V}}$$

b) $P_o = 800 \text{ W}$; $\eta = ?$ $\eta = \frac{P_2}{P_1} = \frac{P_2}{P_2 + P_{cu} + P_o}$

$$P_2 = \sqrt{3} \cdot U_2 \cdot I_2 \cos \varphi_2 = \sqrt{3} \cdot 386 \cdot 125 \cdot 0,8 = 66857 \text{ W}$$

$$P_{cu} = 3 R_k I_2^2 = 3 \cdot 16 \cdot 10^{-3} \cdot 125^2 = 750 \text{ W}$$

$$\eta = \frac{66857}{66857 + 750 + 800} = 0,977 \Rightarrow \underline{\underline{\eta = 97,7\%}}$$


4.

a) Evt. värdedata: $\underline{P_n = 2,2 \text{ kW}}$

$$\underline{P_s = \sqrt{3} \cdot U_n \cdot I_n \cdot \cos \varphi = \sqrt{3} \cdot 400 \cdot 4,9 \cdot 0,7 = 2376,4 \text{ W}}$$

$$\underline{Q_s = \sqrt{3} \cdot U_n \cdot I_n \cdot \sin \varphi = \sqrt{3} \cdot 400 \cdot 4,9 \cdot 0,714 = 2424,4 \text{ VAR}}$$

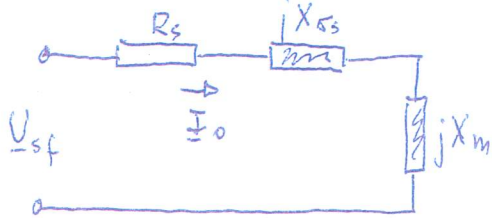b) $Q_o = ?$ $s = 0 \Rightarrow$ eku. schemat:



$$\underline{I_o = \frac{U_{sf}}{R_s + j(X_{\sigma s} + X_m)} = \frac{\frac{400}{\sqrt{3}} \angle 0^\circ}{1,1 + j67,9} = 3,4 \angle -89,1^\circ \text{ A}}$$

$$\underline{Q_o = \sqrt{3} \cdot U_n \cdot I_o \cdot \sin \varphi_o = \sqrt{3} \cdot 400 \cdot 3,4 \cdot \sin 89,1^\circ = 2355 \text{ VAR}}$$

$$\underline{Q_c = Q_o}$$

c) Vattenpumpen: 12 Nm vid 2500 rpm och 6 Nm vid 1000 rpm

$$T - 6 = \frac{12 - 6}{2500 - 1000} (n - 1000)$$

$$T_p = 2 + 0,004n$$


$$\text{AM: } T_n = \frac{P_n}{\omega_n} = \frac{2200}{\frac{2\pi \cdot 1437}{60}} = 14,62 \text{ Nm}$$

0 Nm vid 1500 rpm och 14,62 Nm vid 1437 rpm

$$T_{AM} = 348,1 - 0,232n$$

$$T_p = T_{AM}$$


$$\underline{n = 1466,5 \text{ rpm}}$$

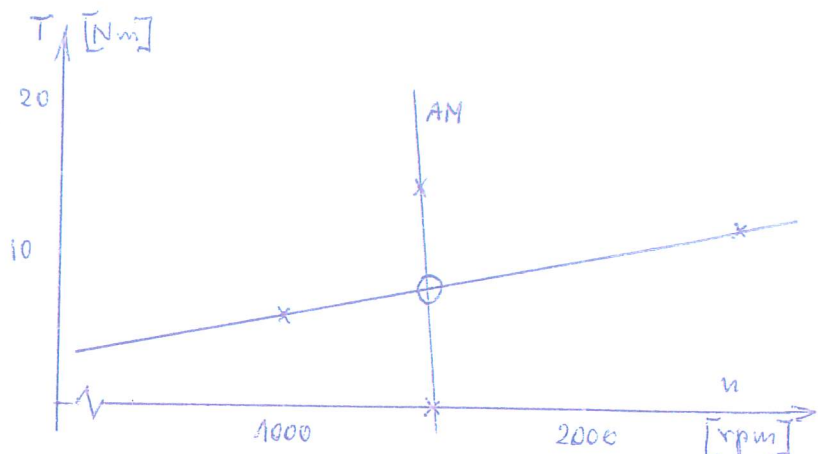

6.

$$U_{\text{batt}} = 96 \text{ V}; I = 10 \text{ A}; U = 300 \text{ V}; T = 0,1 \text{ ms}$$

L och C mycket stora

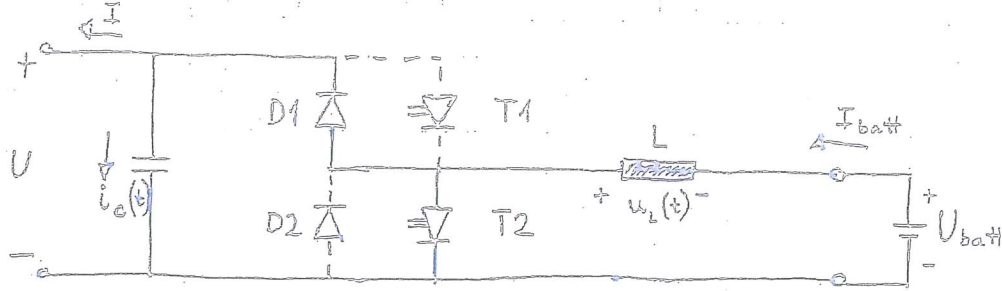

$$a) \frac{t_p}{T} = ?$$


$$0 \leq t < t_p \quad D1$$

$$t_p < t < T \quad T2$$

$$U_{\text{batt}} = \frac{t_p}{T} U$$

$$\frac{t_p}{T} = \frac{96}{300} = \underline{\underline{0,32}}$$

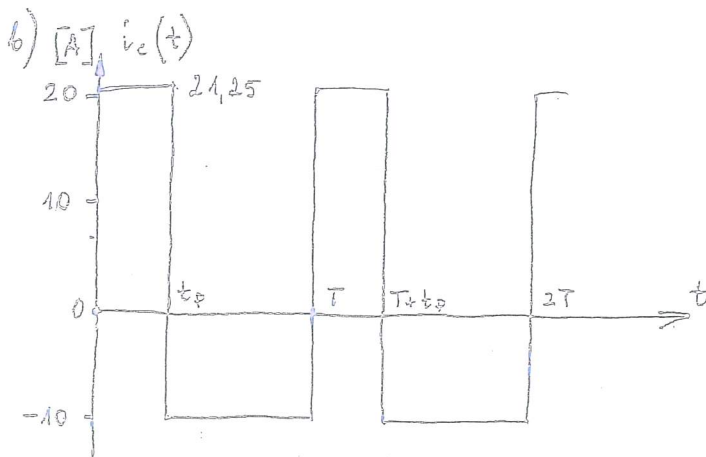
$$t_p = 0,32 \cdot 0,1 = 0,032 \text{ ms}$$



$$U_{\text{batt}} \cdot I_{\text{batt}} = UI$$

$$I_{\text{batt}} = \frac{300}{96} \cdot 10 = 31,25 \text{ A}$$
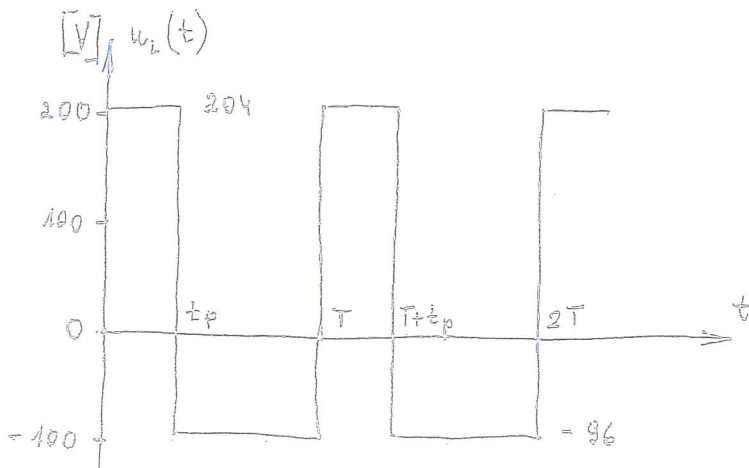
$$i_c(t) = 31,25 - 10 = 21,25 \text{ A}$$



$$u_L = U - U_{\text{batt}} = 300 - 96 = 204 \text{ V} \rightarrow (t_p)$$

$$u_L = -96 \text{ V} \rightarrow (T - t_p)$$

7, $I_k = ?$, $I_s = ?$ vid trefas kortslutning

$$S_{KT} = \frac{S_n}{z_k} = \frac{63 \cdot 10^6}{0,12} = 525 \text{ MVA}$$

$$S_{vänster} = \frac{S_{50kV} \cdot S_{KT}}{S_{50kV} + S_{KT}} = \frac{5000 \cdot 525}{5525} = 475,1 \text{ MVA}$$

I_k på 50 kV skenar: $S_k = S_{vänster} + S_{höger} = 2475,1 \text{ MVA}$

$$I_k = \frac{S_k}{\sqrt{3} \cdot U_k} = \frac{2475,1 \cdot 10^6}{\sqrt{3} \cdot 50 \cdot 10^3} = 28,68 \text{ kA}$$

$$I_s = 2,55 \cdot I_k = 72,88 \text{ kA}$$

