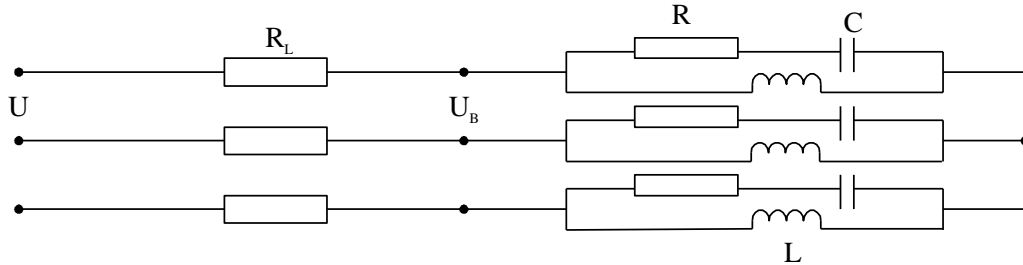


1.


Y-kopplad belastning; $U = 400 \text{ V}$; $f = 50 \text{ Hz}$; $R_L = 0,5 \text{ } \Omega/\text{fas}$

$R = 20 \text{ } \Omega$; $C = 1000 \text{ } \mu\text{F}$; $L = 100 \text{ mH}$

a) $U_B = ?$



Ekvivalent Y-fas-krets :

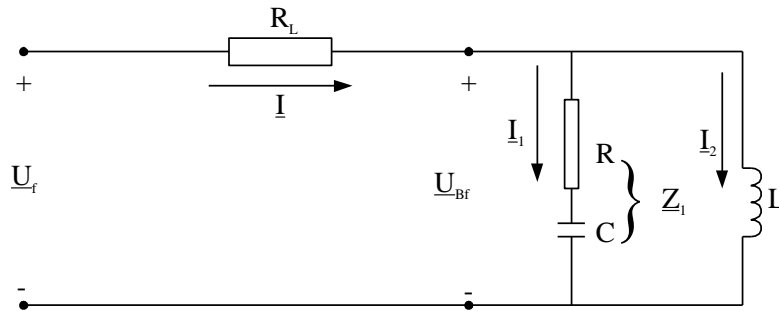

$$U_f - \text{riktfas} \quad U_f = \frac{U}{\sqrt{3}} = \frac{400}{\sqrt{3}} = 230,9 \text{ V}$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi \cdot 50 \cdot 1000 \cdot 10^{-6}} = 3,18 \text{ } \Omega/\text{fas}$$

$$\underline{Z}_1 = 20 - j3,18 = 20,25 \angle -9,03^\circ \text{ } \Omega/\text{fas}$$

$$\underline{Z}_2 = j\omega L = j2\pi \cdot 50 \cdot 100 \cdot 10^{-3} = j31,42 = 31,42 \angle 90^\circ \text{ } \Omega/\text{fas}$$

$$\underline{Z}_B = \underline{Z}_1 // \underline{Z}_2 = \frac{20,25 \angle -9,03^\circ \cdot 31,42 \angle 90^\circ}{20 - j3,18 + j31,42} = 18,39 \angle 26,28^\circ \text{ } \Omega/\text{fas}$$

$$\underline{Z}_{tot} = 0,5 + 16,49 + j8,14 = 18,84 \angle 25,6^\circ \text{ } \Omega/\text{fas}$$

$$\underline{I} = \frac{\underline{U}_f}{\underline{Z}_{tot}} = \frac{230,9 \angle 0^\circ}{18,84 \angle 25,6^\circ} = 12,26 \angle -25,6^\circ \text{ A}$$

$$\underline{U}_{Bf} = \underline{Z}_B \underline{I} = 225,46 \angle 0,68^\circ \text{ V}$$


$$U_B = \sqrt{3} U_{Bf} = 390,5 \text{ V}$$

b) $\underline{I}_1 = ? \quad \underline{I}_2 = ?$

$$\underline{I}_1 = \frac{\underline{U}_{Bf}}{\underline{Z}_1} = \frac{225,46 \angle 0,68^\circ}{20,25 \angle -9,03^\circ} = 11,13 \angle 9,71^\circ \text{ A}$$

$$\underline{I}_2 = \frac{\underline{U}_{Bf}}{\underline{Z}_2} = \frac{225,46 \angle 0,68^\circ}{31,42 \angle 90^\circ} = 7,18 \angle -89,32^\circ \text{ A}$$

c)

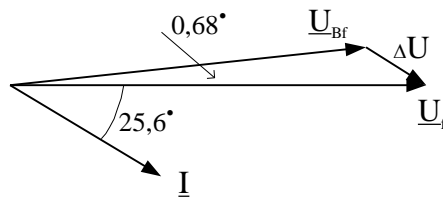

d) $S = ? \quad P = ? \quad Q = ?$

$$\underline{S} = 3 \underline{U}_f \underline{I}^* = 3 \cdot 230,9 \angle 0^\circ \cdot 12,26 \angle 25,6^\circ = 8,49 \cdot 10^3 (0,902 + j0,432) = 7,66 \cdot 10^3 + j3,67 \cdot 10^3$$

$$S = 8490 \text{ VA}$$

$$P = 7660 \text{ W}$$

$$Q = 3670 \text{ VAr}$$

e) $\cos \varphi_B = ?$

$$\cos \varphi_B = \cos 26,28^\circ = 0,897 \quad - \text{ induktiv karaktär}$$

(2)

$$U = 400 \text{ V} ; f = 50 \text{ Hz}$$

Före:



$$P_i = 140 \text{ kW} ; \cos \varphi_i = 0,707$$

$$Q_i = P_i \tan \varphi_i = 140 \text{ kVAR}$$

$$S_i = \sqrt{2} \cdot 140 \text{ kVA} \Rightarrow I_{inf} = \frac{S_i}{\sqrt{3} U} = \frac{\sqrt{2} \cdot 140 \cdot 10^3}{\sqrt{3} \cdot 400} = \underline{\underline{285,5 \text{ A}}}$$

Efter:



$$P_m = 15 \text{ kW} ; P_i = 140 \text{ kW}$$

$$I_m = 28,5 \text{ A} ; Q_i = 140 \text{ kVAR}$$

$$\text{AM} \quad \left\{ \begin{array}{l} S_m = \sqrt{3} \cdot 400 \cdot 28,5 = 19745 \text{ VA} \\ Q_m = \sqrt{S_m^2 - P_m^2} = \sqrt{19745^2 - 15000^2} = 12840 \text{ VAR} \end{array} \right.$$

 Δ -koppl. kond

$$U_c = 400 \text{ V} ; Q_c = 3 \cos C_d U_c^2 = 3 \cdot 100 \cdot 10^{-9} \cdot 1 \cdot 10^{-3} \cdot 400^2 = 150,8 \text{ kVAR}$$

$$Q_{ne} = Q_i + Q_m - Q_c = 140 + 12,84 - 150,8 = 2,04 \text{ kVAR}$$

$$P_{ne} = P_i + P_m = 140 + 15 = 155 \text{ kW}$$

$$\tan \varphi_{ne} = \frac{2,04}{155} \Rightarrow \underline{\underline{\cos \varphi_{ne} = 0,99}}$$

$$I_{ne} = \frac{P_{ne}}{\sqrt{3} U \cos \varphi_{ne}} = \frac{155 \cdot 10^3}{\sqrt{3} \cdot 400 \cdot 0,99} = \underline{\underline{223,7 \text{ A}}}$$

3-fas trafo: $S_n = 40 \text{ kVA}$; $1,5/0,23 \text{ kV}$; D/γ_n

5

a) $z_k = ?$; $r_k = ?$

$U_k = 125 \text{ V}$; $P_k = 550 \text{ W}$; $I_k = I_{1n}$

$$I_k = I_{1n} = \frac{S_n}{\sqrt{3} U_{1n}} = \frac{40 \cdot 10^3}{\sqrt{3} \cdot 1,5 \cdot 10^3} = 15,4 \text{ A}$$

$$R_k = \frac{P_k}{3 I_k^2} = \frac{550}{3 \cdot 15,4^2} = 0,77 \text{ } \Omega/\text{fas} \quad (R'_k = 0,018 \text{ } \Omega/\text{fas})$$

$$Z_k = \frac{U_{kf}}{I_k} = \frac{125}{\sqrt{3} \cdot 15,4} = 4,68 \text{ } \Omega/\text{fas} \Rightarrow X_k = 4,62 \text{ } \Omega/\text{fas}$$

$$(X'_k = 0,11 \text{ } \Omega/\text{fas})$$

$$Z_{bas} = \frac{U_{1n}^2}{S_n} = \frac{(1,5 \cdot 10^3)^2}{40 \cdot 10^3} = 56,25 \text{ } \Omega/\text{fas}$$

$$z_k = \frac{4,68}{56,25} = 0,0832 \quad ; \quad r_k = \frac{0,77}{56,25} = 0,0137$$

$$\underline{z_k = 8,32\%} \quad ; \quad \underline{r_k = 1,37\%}$$

b) $R_{Fe} = ?$; $X_m = ?$

$P_o = 384 \text{ W}$; $I_o = 10 \text{ A}$; $U_o = U_{2n} = 230 \text{ V}$

$$P_{of} = \frac{384}{3} = 128 \text{ W}; \quad R_{Fe} = \frac{U_{of}^2}{P_{of}} = \frac{\left(\frac{230}{\sqrt{3}}\right)^2}{128} = 137,8 \text{ } \Omega/\text{fas}$$

$$Q_{of} = \sqrt{S_{of}^2 - P_{of}^2} = \sqrt{\left(\frac{230}{\sqrt{3}} \cdot 10\right)^2 - 128^2} = 1321,7 \text{ VAR}$$

$$X_m = \frac{U_{of}^2}{Q_{of}} = \frac{\left(\frac{230}{\sqrt{3}}\right)^2}{1321,7} = 13,34 \text{ } \Omega/\text{fas}$$

$R_{Fe} = 137,8 \text{ } \Omega/\text{fas}$; $X_m = 13,34 \text{ } \Omega/\text{fas}$ hänfört till nedsp. sidan

c) $U_2 = ?$; $I_2 = 100 \text{ A}$; $\cos \varphi_2 = 0,8$

$$\Delta U = \sqrt{3} I_2 (R'_k \cos \varphi_2 + X'_k \sin \varphi_2) = \sqrt{3} \cdot 100 (0,018 \cdot 0,8 + 0,11 \cdot 0,6) = 13,93 \text{ V}$$

$$\underline{U_2 = 230 - 13,93 = 216,07 \text{ V}}$$

d) $\underline{P_{cu} = 3 R'_k I_2^2 = 3 \cdot 0,018 \cdot 100^2 = 540 \text{ W}}$

5. AM : $P_n = 15 \text{ kW}$; $U_n = 400 \text{ V}$; $f_n = 50 \text{ Hz}$;
 $I_n = 32 \text{ A}$; $n_n = 970 \text{ rpm}$; $\cos \varphi = 0,81$

a) Motorns momentkurva approximeras med en rät linje
 mellan tomgång och märtdrift

(n=?)

$$T_n = \frac{P_n}{\omega_n} = \frac{15 \cdot 10^3}{\frac{2\pi \cdot 970}{60}} = 147,7 \text{ Nm} ; \quad n_s = 1000 \text{ rpm}$$

vid n_s är $T = 0$

$$T_{AM} = T_n \frac{n_s - n}{n_s - n_n} = 147,7 \frac{1000 - n}{1000 - 970}$$

Lastens momentkurva:

$$T_L = T_{L1} \left(\frac{n}{n_{L1}} \right)^2 \quad T_{L1} = 140 \text{ Nm} \quad \text{vid } n_{L1} = 1000 \text{ rpm}$$

$$T_L = 140 \left(\frac{n}{1000} \right)^2$$


Vid drift gäller : $T_{AM} = T_L$

$$147,7 \frac{1000 - n}{30} = 140 \left(\frac{n}{1000} \right)^2$$

$$n^2 + 35,164 \cdot 10^{-3} n + 35,164 \cdot 10^{-6} = 0$$

$$n = \frac{-35,164 \cdot 10^{-3} \pm \sqrt{(35,164 \cdot 10^{-3})^2 - 4 \cdot 1 \cdot 35,164 \cdot 10^{-6}}}{2}$$


973 rpm

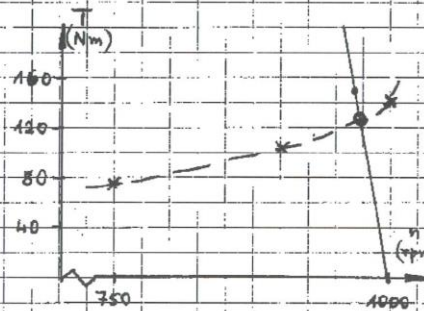

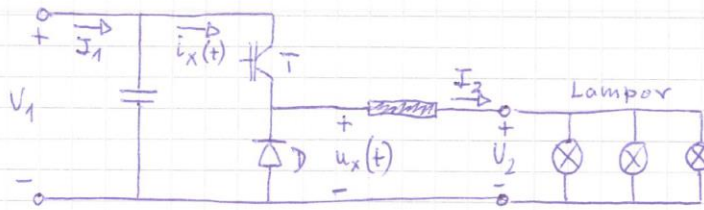
b) $T = 140 \left(\frac{973}{1000} \right)^2 = \underline{\underline{132,5 \text{ Nm}}}$

8


LS-omriktare ; $V_1 = 40\text{ V}$; $T = 50\mu\text{s}$; $V_2 = 12\text{ V}$; $I_2 = 2\text{ A}$



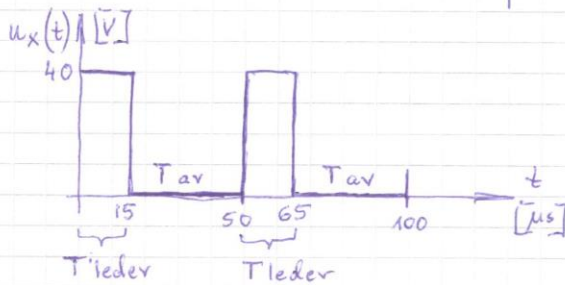a) $t_p = ?$ $u_x(t) = ?$
 b) $V_2 = \frac{t_p}{T} V_1 \Rightarrow t_p = \frac{12}{40} \cdot 50 = 15\mu\text{s}$



c) $i_x(t) = ?$ $I_1 = ?$

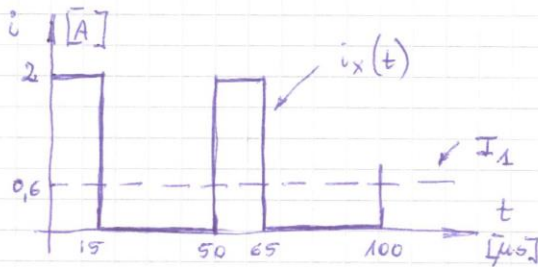

$0 \leq t < t_p$ $i_x = I_2 = 2\text{ A}$
 $t_p \leq t \leq T$ $i_x = 0\text{ A}$

$I_1 V_1 = I_2 V_2 \Rightarrow I_1 = 2 \frac{12}{40} = 0,6\text{ A}$

(9)



$$G1: Z_{G1} = jX_{G1} = j0,2 \cdot \frac{130^2}{75} = j45,1 \text{ } \Omega/\text{fas}$$

$$G2: Z_{G2} = jX_{G2} = j0,22 \cdot \frac{130^2}{60} = j62,0 \text{ } \Omega/\text{fas}$$

$$T1: Z_{T1} = jX_{T1} = j0,1 \cdot \frac{130^2}{75} = j22,5 \text{ } \Omega/\text{fas}$$

$$T2: Z_{T2} = jX_{T2} = j0,08 \cdot \frac{130^2}{60} = j22,5 \text{ } \Omega/\text{fas}$$

$$\text{Linjen: } Z_L = jX_L = j0,4 \cdot 100 = j40,0 \text{ } \Omega/\text{fas}$$

$$\text{Nätet: } Z_N = jX_N = j \frac{130^2}{2000} = j8,45 \text{ } \Omega/\text{fas}$$

$$Z_A = (Z_{G1} + Z_{T1}) // (Z_{G2} + Z_{T2})$$

$$Z_A = jX_A = j \frac{67,6 \cdot 84,5}{152,1} = j37,6 \text{ } \Omega/\text{fas}$$

$$Z_{\text{vänster}} = jX_{\text{vänster}} = j37,6 + j40,0 = j77,6 \text{ } \Omega/\text{fas}$$

$$Z_{\text{höger}} = jX_{\text{höger}} = j8,45 \text{ } \Omega/\text{fas}$$

$$Z_K = Z_v // Z_h \Rightarrow j \frac{77,6 \cdot 8,45}{86,05} = j7,6 \text{ } \Omega/\text{fas}$$

$$\underline{\underline{I_k}} = \frac{U_f}{Z_k} = \frac{130}{\sqrt{3} \cdot 7,6} = \underline{\underline{9,9 \text{ kA}}}$$