

1.

$$U = 400 \text{ V} ; f = 50 \text{ Hz}$$

Belastung I: Y-koppl.; $R = 20$; $C = 100 \mu\text{F}$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi \cdot 50 \cdot 100 \cdot 10^{-6}} = 31,83 \Omega/\text{phas}$$


$$Z_1 = (20 - j31,83) \Omega/\text{phas}$$

Belastung II: Δ -koppl.; $L = 100 \text{ mH}$

$$X_L = \omega L = 2\pi \cdot 50 \cdot 100 \cdot 10^{-3} = 31,42 \Omega$$

$$Z_\Delta = j31,42$$

Ekv. Y-fas:

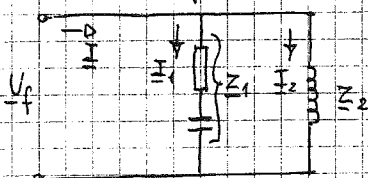

$$Z_2 = \frac{Z_\Delta}{3} = j10,47 \Omega/\text{phas}$$

$$a) \underline{I}_1 = \frac{U_f}{Z_1} = \frac{\frac{400}{\sqrt{3}} \angle 0^\circ}{20 - j31,83} = \frac{\frac{400}{\sqrt{3}} \angle 0^\circ}{37,59 \angle -57,86^\circ} = \underline{6,14 \angle 57,86^\circ} = \underline{(3,27 + j5,2) \text{ A}}$$

$$\underline{I}_2 = \frac{U_f}{Z_2} = \frac{\frac{400}{\sqrt{3}} \angle 0^\circ}{j10,47} = \underline{22,05 \angle -90^\circ \text{ A}}$$

$$\underline{I} = \underline{I}_1 + \underline{I}_2 = 3,27 + j5,2 - j22,05 = 3,27 - j16,85 = \underline{17,16 \angle -79^\circ \text{ A}}$$


$$|\underline{I}_\Delta| = \frac{|\underline{I}_2|}{\sqrt{3}} \Rightarrow |\underline{I}_\Delta| = \underline{12,73 \text{ A}}$$

c) Belastung I - kap. charakter

Belastung II - ind. charakter

Totallasten - ind. charakter
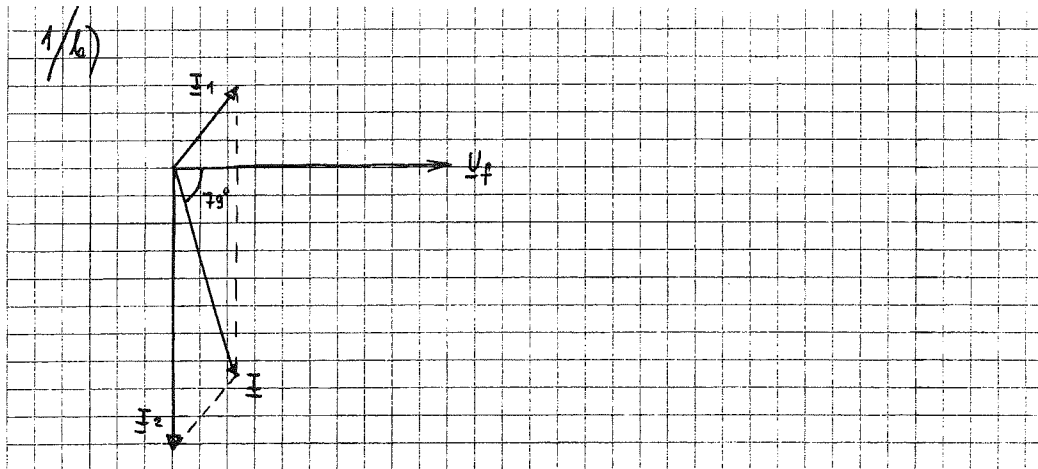
$$d) \underline{S} = 3 U_f \underline{I}^* = 3 \cdot \frac{400}{\sqrt{3}} \angle 0^\circ \cdot 17,16 \angle 79^\circ = 11,89 \cdot 10^3 \angle 79^\circ = \underline{(2269 + j1167,2) \text{ VA}}$$



2 a)

1. Före inkoppling av AM och C:

$$U = 400 \text{ V}; f = 50 \text{ Hz}; P_i = 140 \text{ kW}; \cos \varphi_i = 0,707$$

$$\Rightarrow Q_i = 140 \text{ kVAR} \Rightarrow S_i = \sqrt{P_i^2 + Q_i^2} = \sqrt{2} \cdot 140 \text{ kVA}$$

$$I = \frac{S_i}{\sqrt{3} U} = \frac{\sqrt{2} \cdot 140 \cdot 10^3}{\sqrt{3} \cdot 400} = \underline{\underline{285,8 \text{ A}}}$$

2. Efter inkoppling av AM och C:

$$Q_c = 3 \omega C U_c^2; U_c = U = 400 \text{ V}; C = 1 \cdot 10^{-3} \text{ F}$$

$$Q_c = 3 \cdot 100 \pi \cdot 1 \cdot 10^{-3} \cdot 400^2 = 150,8 \text{ kVAR}$$

$$P_m = 15 \text{ kW}; I_m = 28,5 \text{ A} \Rightarrow S_m = \sqrt{3} \cdot 400 \cdot 28,5 = 19,75 \text{ kVA}$$

$$Q_m = \sqrt{S_m^2 - P_m^2} = 12,84 \text{ kVAR}$$

Från nätet:


$$P = P_i + P_m = 140 + 15 = 155 \text{ kW}$$

$$Q = Q_c + Q_m - Q_i = 140 + 12,84 - 150,8 = 2,04 \text{ kVAR}$$

$$I = \frac{S}{\sqrt{3} \cdot U} = \frac{\sqrt{155^2 + 2,04^2} \cdot 10^3}{\sqrt{3} \cdot 400} = \underline{\underline{223,7 \text{ A}}}$$

$$\underline{\underline{\cos \varphi = \frac{P}{S} = \frac{155}{155,01} \approx 1}}}$$

4.

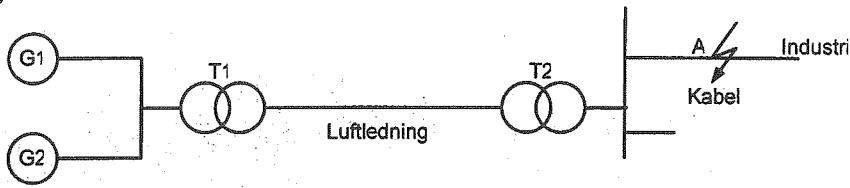

a) Imp. sum. metoden: $U_c = 20 \text{ kV}$

$$\text{Gen 1 och Gen 2} \Rightarrow X_d = x_d \frac{U_c^2}{S_n} = 0,2 \frac{20^2}{25} = 3,2 \text{ } \Omega/\text{fas}$$

$$\Rightarrow X_G = \frac{X_d}{2} = 1,6 \text{ } \Omega/\text{fas}$$

Trafo T1:

$$R_{T1} = r_k \frac{U_c^2}{S_n} = 0,02 \frac{20^2}{50} = 0,16 \text{ } \Omega/\text{fas}$$

$$Z_{T1} = z_k \frac{U_c^2}{S_n} = 0,12 \frac{20^2}{50} = 0,96 \text{ } \Omega/\text{fas}$$

$$X_{T1} = \sqrt{Z_{T1}^2 - R_{T1}^2} = 0,947 \text{ } \Omega/\text{fas}$$

Trafo T2:

$$R_{T2} = 0,01 \frac{20^2}{50} = 0,08 \text{ } \Omega/\text{fas}$$

$$Z_{T2} = 0,1 \frac{20^2}{50} = 0,8 \text{ } \Omega/\text{fas}$$

$$X_{T2} = 0,796 \text{ } \Omega/\text{fas}$$

Luftledning:
130kV

$$40 \text{ km} \quad R_L = 0,15 \cdot 40 \cdot \left(\frac{20}{130}\right)^2 = 0,142 \text{ } \Omega/\text{fas}$$

$$X_L = 0,4 \cdot 40 \cdot \left(\frac{20}{130}\right)^2 = 0,379 \text{ } \Omega/\text{fas}$$

Kabel:
20kV

$$1 \text{ km} \quad R_K = 0,05 \text{ } \Omega/\text{fas}; \quad X_K = 0,1 \text{ } \Omega/\text{fas}$$

$$\sum R = 0,16 + 0,08 + 0,142 + 0,05 = 0,432 \text{ } \Omega/\text{fas}$$

$$\sum X = 1,6 + 0,947 + 0,796 + 0,379 + 0,1 = 3,82 \text{ } \Omega/\text{fas}$$

$$Z = \sqrt{R^2 + X^2} = 3,846 \text{ } \Omega/\text{fas}$$

$$\underline{\underline{I_k = \frac{U_f}{Z} = \frac{20 \cdot 10^3}{\sqrt{3} \cdot 3,846} = 3002 \text{ A}}}$$

4b)

$$I = 650 \text{ A} ; \cos \varphi = 0,8$$

$$\begin{array}{l} T2 \quad R_k = 0,08 \text{ } \Omega/\text{fas} \\ \quad \quad X_k = 0,796 \text{ } \Omega/\text{fas} \end{array} \left. \begin{array}{l} \text{h} \ddot{a} \text{r f} \ddot{o} \text{r} \\ \text{till } 20 \text{ kV} \text{ i} \text{sidan} \end{array} \right\}$$

$$\begin{aligned} \Delta U &= \sqrt{3} I (R_k \cos \varphi + X_k \sin \varphi) = \\ &= \sqrt{3} \cdot 650 (0,08 \cdot 0,8 + 0,796 \cdot 0,6) = \underline{\underline{609,75 \text{ V}}} \end{aligned}$$

$$\underline{\underline{U_0 = 20000 - 609,75 = 19390,25 \text{ V}}}$$

6.

3-fas AM: 150 kW; 3,3 kV; 36 A; $\cos\varphi = 0,8$
 965 rpm; 50 Hz; $R_s = 1,5 \Omega/\text{fas}$

$$P_{\text{start}} = 345 \text{ kW}; I_{\text{start}} = 200 \text{ A}$$

a) $T_{\text{start}} = ?$

Vid start gäller $s = 1$

P_m och P_{Fes} kan försummas \Rightarrow

$$P_m = P_{\text{Fes}} = 0 \Rightarrow P_s = P_g + P_{\text{cus}}$$

$$P_{\text{cus}} = 3 R_s I_{\text{start}}^2 = 3 \cdot 1,5 \cdot 200^2 = 180 \text{ kW}$$

$$P_g = P_{\text{start}} - P_{\text{cus}} = 345 - 180 = 165 \text{ kW}$$

$$T_{\text{start}} = \frac{P_g}{\omega_s} = \frac{165 \cdot 10^3}{\frac{2\pi \cdot 965}{60}} = 1575,6 \text{ Nm}$$

b) $T_n = ?$


$$T_n = \frac{P_n}{\omega_n} = \frac{150 \cdot 10^3}{\frac{2\pi \cdot 965}{60}} = 1484,3 \text{ Nm}$$

$$\frac{T_{\text{start}}}{T_n} = \frac{1575,6}{1484,3} = 1,06$$

c) $P_{\text{cusin}} = 3 \cdot 1,5 \cdot 36^2 = 5832 \text{ W}$


$$\frac{P_{\text{cusstart}}}{P_{\text{cusin}}} = \frac{180000}{5832} = 30,86 \text{ ggr}$$

d)

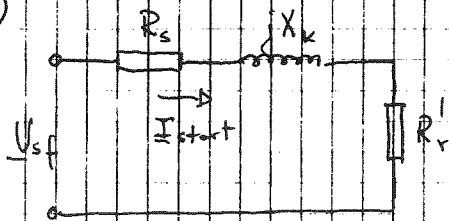

8)

a)

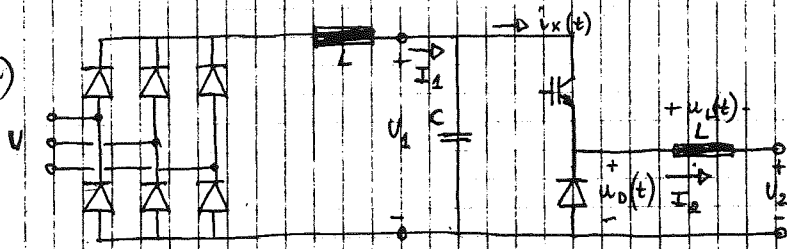

3-fas diadliktare

LS-omviktaven

$$U = 400 \text{ V} \Rightarrow U_2 = 1,35 U = 540 \text{ V}$$

$$f = 50 \text{ kHz}$$


$$U_2 = 250 \text{ V}; I_2 = 10 \text{ A}$$

b)

$$\frac{U_2}{U_1} = \frac{t_p}{T}$$


$$T = \frac{1}{f} = 20 \cdot 10^{-6} \text{ s}; t_p = \frac{U_2}{U_1} T = \frac{250}{540} \cdot 20 \cdot 10^{-6} = 9,26 \mu\text{s}$$

$$u_c(t) = ?$$

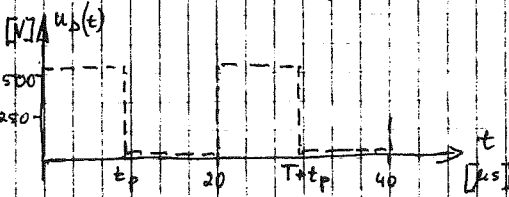

c)

$$u_L(t) = ?$$

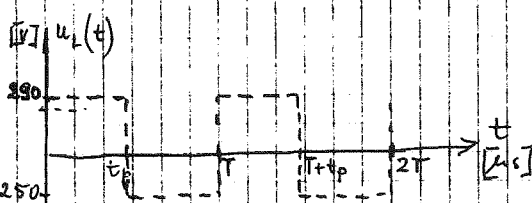

d)

$$U_1 I_1 = U_2 I_2$$

$$I_1 = \frac{U_2}{U_1} I_2 = \frac{250}{540} \cdot 10 = 4,63 \text{ A}$$

