

Examination**ENM060 Power Electronic Converters****Date and time**Tuesday August 23rd, 2016, 14:00 – 18:00**Responsible Teacher:**

Andreas Henriksson, tel. 0709-524924

Authorised Aids:

Chalmers-approved calculator (Casio FX82..., Texas Instruments Ti-30... and Sharp EL-W531...)

Grades:

U, 3, 4 or 5. (The limit for a 3 on the exam is 20p, a 4 is 30p and 5 is 40p. The maximum number of points is 50.)

Solutions:Course webpage (Ping-Pong), August 24th 2016**Review of Exam**September 15th and September 19th, 12:00-13:00.Uno Lamms Room. Division of Electric Power Engineering (2nd floor).From September 20th 2016, the exams can be picked-up at the exam office, Department of Energy and Environment.

Location: EDIT building, Maskingränd 2, 3Ö (east) floor, room 3434A.

Opening hours during semesters: Monday-Friday 12:30-14:30



Observe that the questions are not arranged in any kind of order.

On the last pages there are some formulas that can be used in the examination. Always assume steady-state conditions in all tasks unless otherwise stated.

Please, read through the exam before you start.

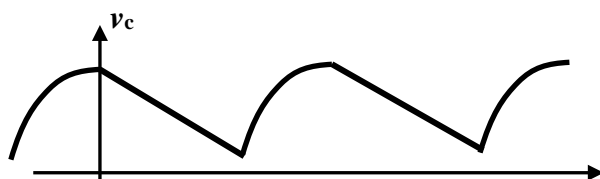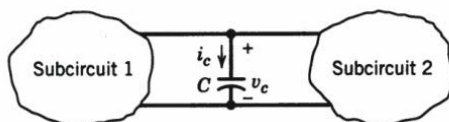1) **The voltage curve-form (v_c) is applied over the capacitor which are connected to two arbitrary sub-circuits. (3p)**

- **Explain the concept of steady state.**
- **Sketch the resulting current that flows into the capacitor (i_c).**




2) Consider the ideal boost converter below.

- Calculate the peak-to-peak output voltage ripple for the specified operating point.
- Draw the curve form of the voltage ripple. (5p)


$$V_d = 8V \quad V_o = 12V \quad I_o = 6A$$
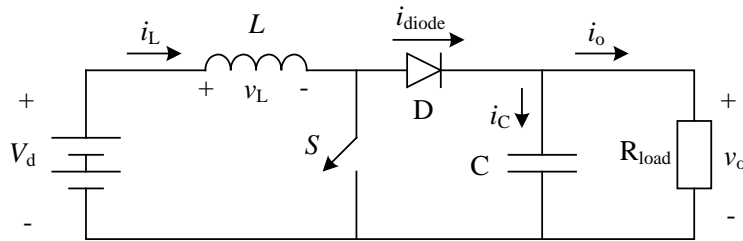
$$f_{sw} = 320kHz \quad C = 270\mu F \quad L = 1.4\mu H$$



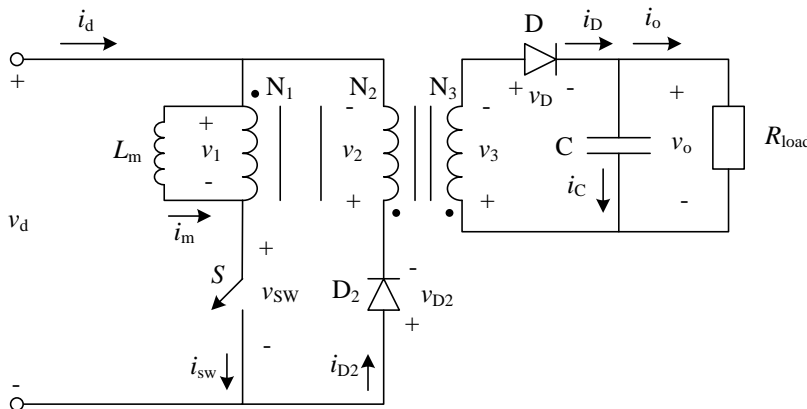3) Consider the Flyback converter below. (5p)

- For the given operating point, check if the converter is operating in CCM or DCM.
- Calculate the resulting temperature of the output diode (D) if the ambient temperature is 30°C. Application of Simpsons formula must be used for full points.



$$L_m = 120\mu H$$

$$C = 330\mu F$$

$$V_d = 20V$$

$$V_o = 32V$$

$$f_{sw} = 250kHz$$

$$R = 4\Omega$$


$$(N_1 : N_2 : N_3) = (1 : 0.5 : 1)$$

$$V_f = 0.84V$$

$$R_{\theta ja} = 10^\circ C/W$$

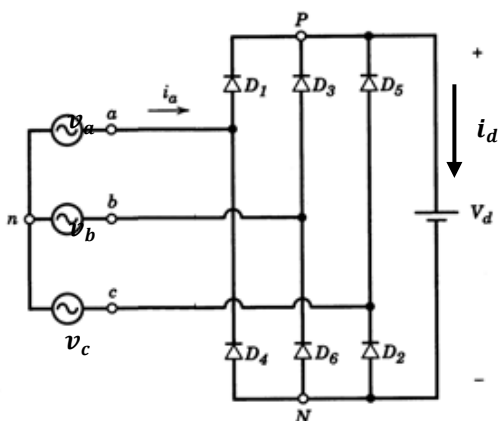
4) The three phase diode rectifier depicted below is used with a voltage stiff DC-link. The system operates with 50Hz and $v_a = v_b = v_c = 230V$ peak voltage. Draw the voltages and currents stated below. Clearly state the amplitudes and phase shifts between the voltages, exact amplitudes of the currents are not needed. (5p)

- The phase voltage in phase a (v_{an})
- The line-to-line voltages for phase a (v_{ab} and v_{ac})
- The current in phase a (i_a).
- The DC-side current (i_d).




- 5) A single-phase diode rectifier with a voltage stiff DC-side (large DC-link capacitor) is connected to a grid with a source inductance. (4p)
- Sketch a typical waveform of the resulting line current (i_s)
 - How will the source inductance affect the power factor (PF) and the displacement power factor (DPF)? Exemplify with e.g. graphs and Fourier components.

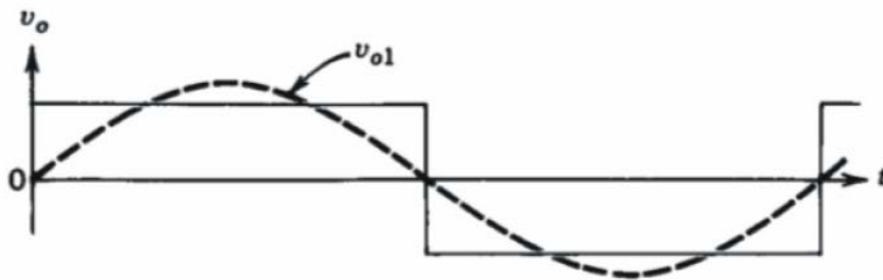- 6) For a single phase inverter operating in square wave mode, calculate the peak-to-peak ripple in the output current. Assume that the fundamental frequency component of the output voltage is $v_{o(1)} = 156V$ (50Hz) and that the load consists of an inductor ($L = 100mH$) in series with a sinusoidally shaped back-emf voltage source ($e_o = \sqrt{2} \cdot E_o \cdot \sin(\omega_1 t)$). The back-emf has the same amplitude, frequency and phase shift as the fundamental frequency component of the output voltage. The DC-link voltage (V_d) is 170V. (5p)




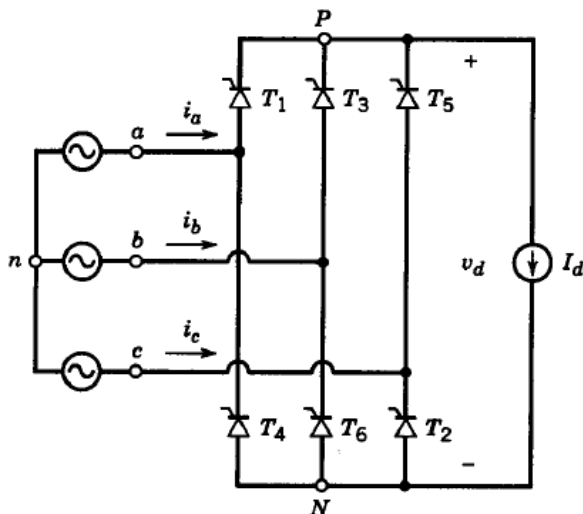- 7) A three-phase thyristor inverter is operating with a constant current load ($I_d = 25A$). The three-phase network is assumed to be a balanced system with no line impedance. (4p)
- Draw the voltage waveforms (v_{Nn} , v_{Pn} , v_d) for $\alpha = 150^\circ$ on the enclosed dot-paper.
 - Draw the current waveforms (i_a , i_b , i_c) and state the amplitude.



- 8) For the Thyristor inverter in (7), each component is turned on by applying a pulse on the gate terminal. (3p)
- Is the thyristor a current or voltage controlled device?
 - Explain why it could be a problem to operate this inverter with large firing angles (large α), for example 180° .

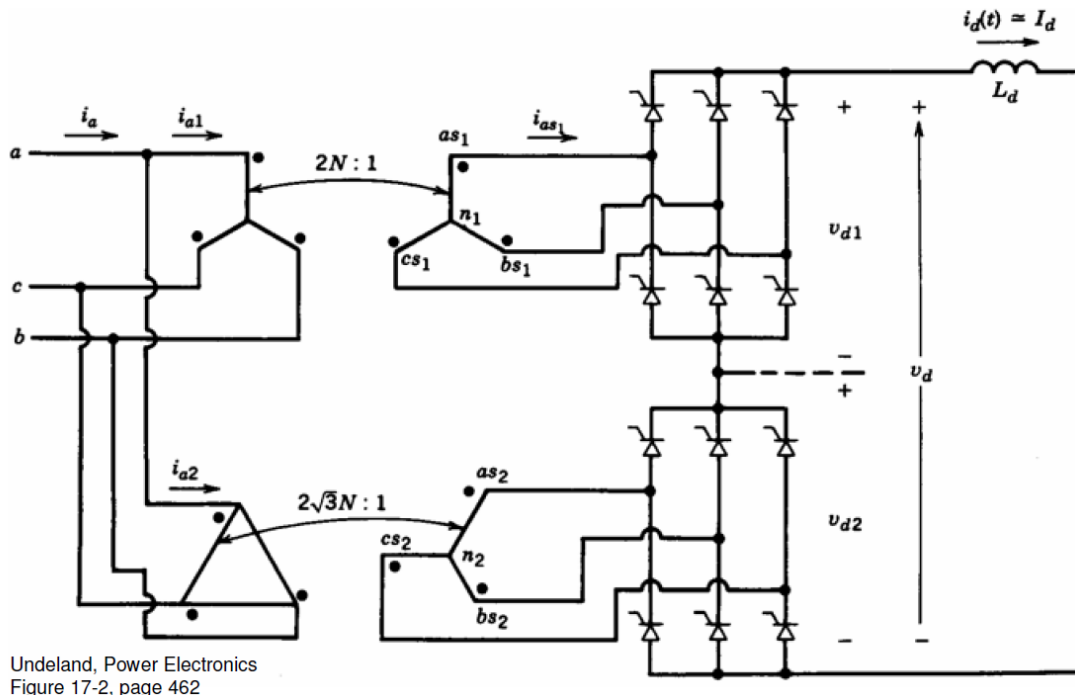- 9) Heat can be transferred by three different mechanisms and it is important to design your application so that it does not become too hot. If a semiconductor becomes too hot and is exposed to extensive thermal cycling, it will eventually break down. (4p)
- Which are the three heat transfer mechanisms and which one is the most important in semiconductors for power electronic applications?
 - What is the typical reason for component failure in a semiconductor for power electronic applications?
- 10) What are the main benefits of using 12-pulse rectification in a three-phase thyristor application (e.g. a HVDC classic)? Exemplify with e.g. input current and output voltage. (4p)



- 11) A Flyback converter with two secondary windings (i.e. two output voltages v_{01} and v_{02}) is used with real components including parasitic elements. The controller circuit only regulates one output voltage (v_{01}). Explain thoroughly what happens if a load step (e.g. sudden increase/decrease of the output current) is applied on output v_{01} and v_{02} , respectively. (4p)
- 12) Compare the transformer utilization for a flyback, forward and a full-bridge. Comment on how the transformer is used in each converter, i.e. advantages/disadvantages. (4p)

	Flyback	Forward	Full-bridge
Transformer utilization			
Comment			

Formulas for Examination in Power Electronic Converters (ENM060)

Table 3-1 Use of Symmetry in Fourier Analysis

Symmetry	Condition Required	a_h and b_h	
Even	$f(-t) = f(t)$	$b_h = 0$	$a_h = \frac{2}{\pi} \int_0^{\pi} f(t) \cos(h\omega t) d(\omega t)$
Odd	$f(-t) = -f(t)$	$a_h = 0$	$b_h = \frac{2}{\pi} \int_0^{\pi} f(t) \sin(h\omega t) d(\omega t)$
Half-wave	$f(t) = -f(t + \frac{1}{2}T)$	$a_h = b_h = 0$ for even h $a_h = \frac{2}{\pi} \int_0^{\pi} f(t) \cos(h\omega t) d(\omega t)$ for odd h $b_h = \frac{2}{\pi} \int_0^{\pi} f(t) \sin(h\omega t) d(\omega t)$ for odd h	
Even quarter-wave	Even and half-wave	$b_h = 0$ for all h	$a_h = \begin{cases} \frac{4}{\pi} \int_0^{\pi/2} f(t) \cos(h\omega t) d(\omega t) & \text{for odd } h \\ 0 & \text{for even } h \end{cases}$
Odd quarter-wave	Odd and half-wave	$a_h = 0$ for all h	$b_h = \begin{cases} \frac{4}{\pi} \int_0^{\pi/2} f(t) \sin(h\omega t) d(\omega t) & \text{for odd } h \\ 0 & \text{for even } h \end{cases}$

Definition of RMS-value:

$$F_{RMS} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} f(t)^2 dt}$$

Definition of RMS-value with Fourier-series:

$$F_{RMS} = \sqrt{F_0^2 + \sum_{n=1}^{\infty} F_n^2} = \sqrt{\left(\frac{\alpha_0}{2}\right)^2 + \sum_{n=1}^{\infty} \left(\frac{\sqrt{a_n^2 + b_n^2}}{\sqrt{2}}\right)^2}$$

$$\sin^2(\alpha) + \cos^2(\alpha) = 1$$

$$\sin(\alpha + \beta) = \sin(\alpha) \cos(\beta) + \cos(\alpha) \sin(\beta)$$

$$\cos(\alpha + \beta) = \cos(\alpha) \cos(\beta) - \sin(\alpha) \sin(\beta)$$

$$\sin(\alpha) \sin(\beta) = \frac{1}{2} (\cos(\alpha - \beta) - \cos(\alpha + \beta))$$

$$\cos(\alpha) \cos(\beta) = \frac{1}{2} (\cos(\alpha - \beta) + \cos(\alpha + \beta))$$

$$\int \sin(ax) dx = -\frac{1}{a} \cos(ax), \quad \int x \sin(ax) dx = \frac{1}{a^2} (\sin(ax) - ax \cos(ax)), \quad \int \cos(ax) dx = \frac{1}{a} \sin(ax)$$

$$\int x \cos(ax) dx = \frac{1}{a^2} (\cos(ax) + ax \sin(ax))$$

$$PF = \frac{P}{S} = \frac{V_s I_{s1} \cos \phi_1}{V_s I_s}, \quad DPF = \cos \phi_1, \quad \%THD_i = 100 \frac{I_{dis}}{I_{s1}} = 100 \frac{\sqrt{I_s^2 - I_{s1}^2}}{I_{s1}} = 100 \sqrt{\sum_{h \neq 1} \left(\frac{I_{sh}}{I_{s1}}\right)^2}$$

Electromagnetics

$$e = \frac{d}{dt} \psi \quad \psi = N\phi \quad \phi = BA \quad R = \frac{l}{A\mu_r\mu_0} \quad L = \frac{\Psi}{i}$$

$$NI = R\phi = mmf \quad N\phi = LI \quad L = A_L N^2 \quad W = \frac{1}{2} LI^2$$

Simpson's rule

Let $f(x)$ be a polynomial of maximum third degree, this means

$$f(x) = a_1 + a_2 x + a_3 x^2 + a_4 x^3$$

For this function the integral can be calculated as

$$\frac{1}{T} \int_{t_0}^{t_0+T} f(x) dx = \frac{1}{6} \left(f(t_0) + 4f\left(t_0 + \frac{T}{2}\right) + f(t_0 + T) \right)$$

