

1. (a) & (b) check lecture handouts (2 pts each part)

2.  $V_o = 12V$   $P_o = 48W$   $V_d = 18V$   $f_{sw} = 20kHz$

2(a) Boundary condition  $\Rightarrow$  CCM and  $I_L = \frac{1}{2} \hat{\Delta i_L}$

$I_o = P_o / V_o = 4A \Rightarrow R = V_o / I_o = 3\Omega$

$$\left. \begin{array}{l} \text{during off-period, } V_L = -V_o \\ \text{during on-period, } V_L = V_d \end{array} \right\} \Rightarrow V_{L=0} = V_d \cdot D - V_o(1-D) = 0$$

$\Rightarrow \frac{V_o}{V_d} = \frac{D}{1-D} \Rightarrow D = \underline{\underline{0.4}}$

$P_o = P_{in} \Rightarrow V_d I_d = P_o \Rightarrow I_d = \underline{\underline{2.67A}} \quad (1)$


using  $i_L = i_d + i_{diode} \Rightarrow \hat{I}_L = I_d + I_{diode} = I_d + I_o = \underline{\underline{6.67A}}$

$\Rightarrow \hat{\Delta i_L} = 2\hat{I}_L = \underline{\underline{13.34A}} \quad (1)$

during on period,  $V_L = V_d: \frac{L \hat{\Delta i_L}}{DT_s} = \frac{L f_{sw} \hat{\Delta i_L}}{D}$

$\Rightarrow L = \frac{DV_d}{f_{sw} \hat{\Delta i_L}} = \underline{\underline{27\mu H}} \quad (2)$

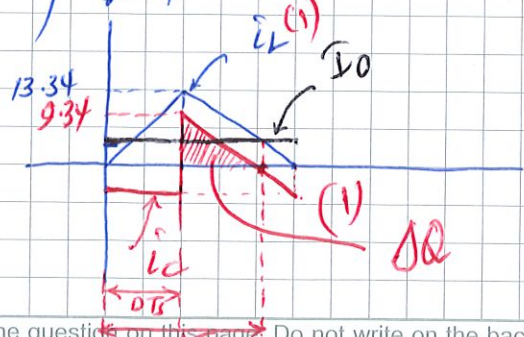2(b) during on period,  $i_c = -I_o$ ; during off period,  $i_c = i_L - I_o$



the time  $i_c = 0$  is calculated when  $i_L = I_o$

$$\Rightarrow \frac{\Delta - D}{\hat{\Delta i_L} - I_o} = \frac{1-D}{\hat{\Delta i_L}}$$

$$\Rightarrow \Delta = \underline{\underline{0.8262}}$$




$$2(c) \Delta Q = \frac{1}{2} (\Delta - D) T_s \cdot \hat{i}_c \quad (1)$$

$$\Rightarrow \Delta V_o = \Delta Q / C = \frac{(\Delta - D) \hat{i}_c}{2 f_{sw} \cdot C}$$

$$\Rightarrow C_{min} = \frac{(\Delta - D) \hat{i}_c}{2 f_{sw} \cdot \Delta V_o} = \begin{cases} 40.9 \text{ MF} & \text{for } 10\% \text{ ripple} \\ 409 \text{ MF} & \text{for } 1\% \text{ ripple} \end{cases}$$

(1)

2(d)

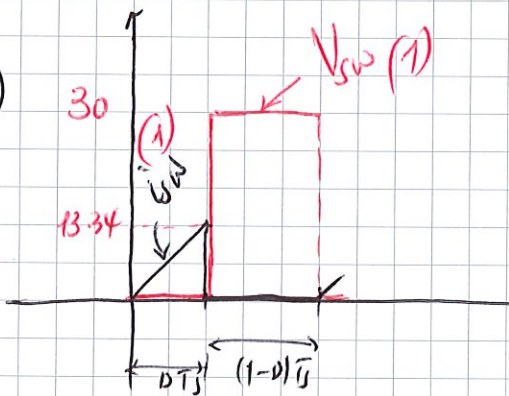

$i_{sw} = i_d = i_L$  during on, 0 during off

$V_{sw} = 0$  during on

$$V_{sw} = V_d - V_L = V_d + V_o = 30V$$

3.  $N_1 : N_2 : N_3 = 1 : 2 : 2$  ;  $V_d = 20V$  ,  $f_{sw} = 20 \text{ kHz}$  ,  $D = 0.3$  ,  $L_m = 100 \mu\text{H}$

3(a).  $R_{load} = 20 \Omega$  ,  $V_o = ?$

Assume CCM  $\Rightarrow V_o = \frac{N_3 D}{N_1 (1-D)} V_d = \frac{2}{1} \cdot \frac{0.3}{1-0.3} \cdot 20V = \underline{\underline{17.143V}}$

$$V_{o,max} = \frac{N_3}{N_2} V_d = 20V > V_o \quad (N_2 \text{ winding not used})$$

$$I_D = I_o = \frac{V_o}{R_{load}} = \frac{17.143}{20} \text{ A} = \underline{\underline{0.858 \text{ A}}}$$

$$I_d = P_o / V_d = V_o I_o / V_d = \underline{\underline{0.7354 \text{ A}}}$$

(1)

$$\Rightarrow I_m = I_d + \frac{N_3}{N_1} I_o = (0.735 + 2(0.858)) \text{ A} = \underline{\underline{2.451 \text{ A}}}$$

During on-period,  $L_m \frac{\Delta i_m}{\Delta T_s} = V_d \Rightarrow \Delta i_m = \frac{D V_d}{L_m f_{sw}} \text{ A} = 3 \text{ A}$

$$\frac{\Delta i_m}{2} \leq 1.5 \text{ A} < I_m = 2.45 \text{ A} \Rightarrow \text{Converter in CCM.} \quad (1)$$








4. (a)

$$V_1 = -V_d \quad (1)$$

$$V_{D1} = -2N_2/N_1 V_d \quad (1) \quad (D_1 = \text{off})$$
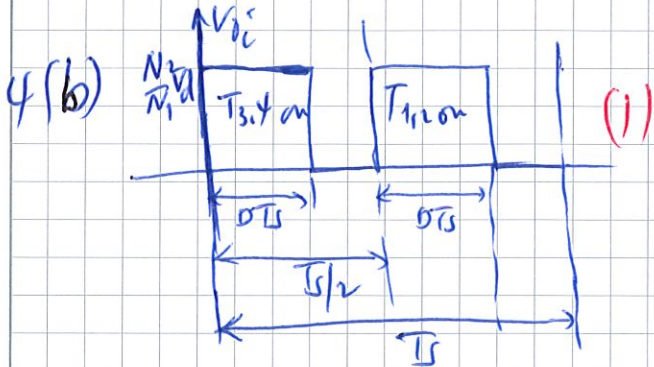
$$V_{D2} = 0 \quad (1) \quad (D_2 = \text{on})$$



$$V_o = \frac{1}{T_s} \int_0^{T_s} V_{2i} dt = 2 \left( \frac{N_2}{N_1} \right) \cdot 0.5 \cdot V_d \cdot \frac{1}{T_s} \cdot T_s$$

$$V_o = 2 \frac{N_2 D}{N_1} \cdot V_d$$

$$\frac{V_o}{V_d} = 2 \frac{N_2 D}{N_1} \quad (1)$$

5. (a) check lecture notes for  $V_{No}$  and  $V_A$ .  
for sensitive load,  $i_A = V_A / R_{load} = V_A / 30 \Omega$  (1)

5. (b)  $I_d = P_o / V_d$  where  $P_o = 3 \frac{1}{T_s} \int_0^{T_s} V_A \cdot i_A dt$

$$= 3 \cdot \frac{1}{2\pi} \int_0^{2\pi} V_A^2 / 30 d\theta$$

2)  $I_d = \frac{3}{2\pi V_d} \int_0^{2\pi} V_A^2 dt$  (1)


dc harmonics : square wave  $\rightarrow$  low order (1)  
PWM  $\rightarrow$  high order harmonics (1)

5. (c) PWM,  $\hat{V}_{A(1)} = m_a \cdot V_d / 2 = V_d / 2 \text{ V} = 150 \text{ V}$  (1)

square wave  $\hat{V}_{A(1)} = \frac{4}{\pi} \cdot \frac{V_d}{2} \text{ V} = 191 \text{ V}$  (using Fourier) (2)



6.(a)

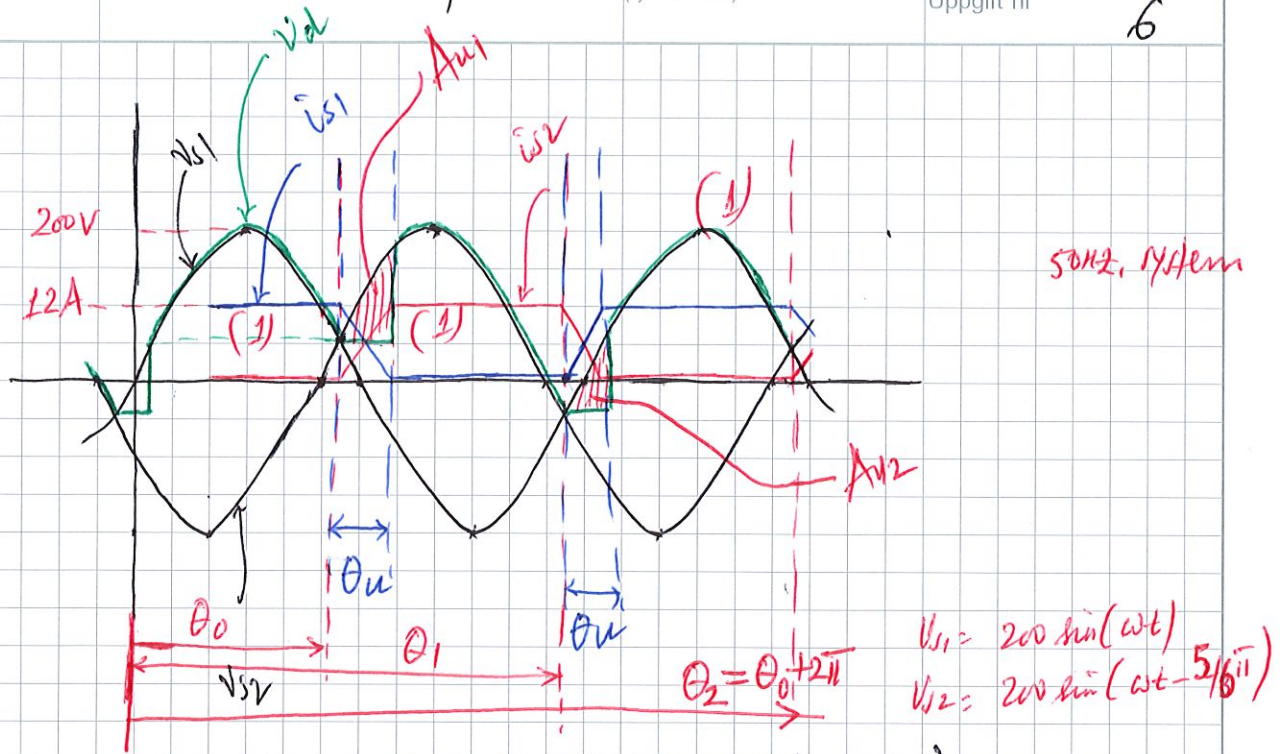

at  $\theta_0 : v_{s1} = v_{s2} \Rightarrow 200 \sin(\theta_0) = 200 \sin(\theta_0 - 5/6\pi)$   
 $\Rightarrow \sin(\theta_0) = \sin(\theta_0 - 5/6\pi)$ ,  $\pi/2 < \theta_0 < \pi$   
 $\Rightarrow \theta_0 = ?$   
 Find also  $\theta_1$  where  $\sin(\theta_1) = \sin(\theta_1 - 5/6\pi)$   
 $3/2\pi < \theta_1 < 2\pi$

6(b) look 6(a) for plot of  $v_d$

Find  $\theta_0$  and  $\theta_1$  and show  $v_d$  calculation

then 
$$V_d = \frac{1}{2\pi} \int_{\theta_0}^{\theta_0 + 2\pi} v_d \cdot dt = \frac{1}{2\pi} \left[ \int_{\theta_0 + \theta_u}^{\theta_1} v_{s1} dt + \int_{\theta_1 + \theta_u}^{\theta_1 + 2\pi} v_{s2} dt - A_{u1} - A_{u2} \right]$$

$\theta_u = ?$  and then  $v_d = ?$  during commutation


$$v_d = v_{s1} - L_s \frac{di_1}{dt} = v_{s2} - L_s \frac{di_2}{dt} \quad \left( i_2 = i_1 - i_u \right) \quad v_d = \frac{v_{s1} + v_{s2}}{2}$$

$$\Rightarrow v_{s1} - v_{s2} = 2L_s \frac{di_1}{dt} \Rightarrow L_s \frac{di_1}{dt} = \frac{v_{s1} - v_{s2}}{2} \Rightarrow v_d = ?$$

$\theta_u$  is calculated from  $i_2$  goes from  $I_d$  to 0

Dot paper for Question 7 (give a page number and put this paper together with your answer sheets if you use it for your answers. The distance between the dots in the voltage plots is  $5^\circ$ .)


1) Phase-voltage plot for part 7.a.

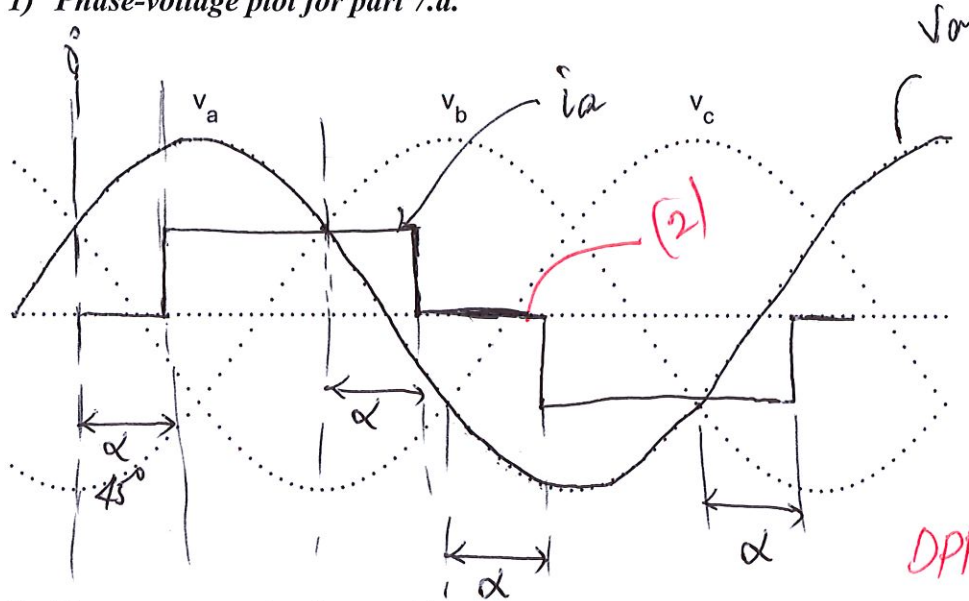


(1)  
 $DPF = \cos(\alpha)$

2) Phase-current plot for part 7.a.

See Fig. above

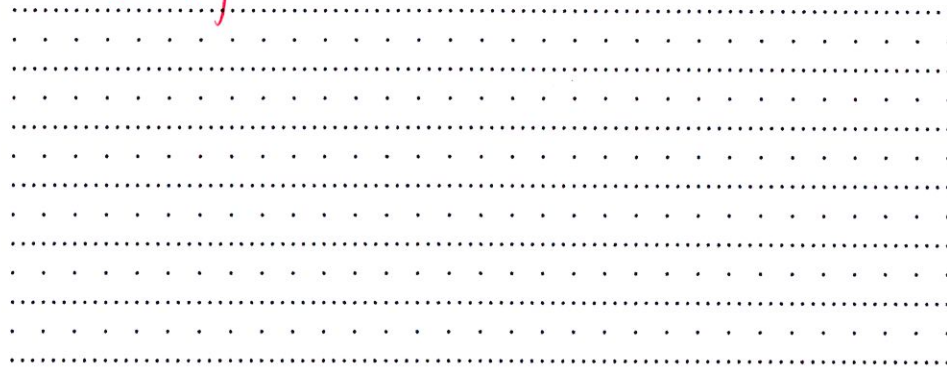

3) Output dc-voltage plot for part 7.b.

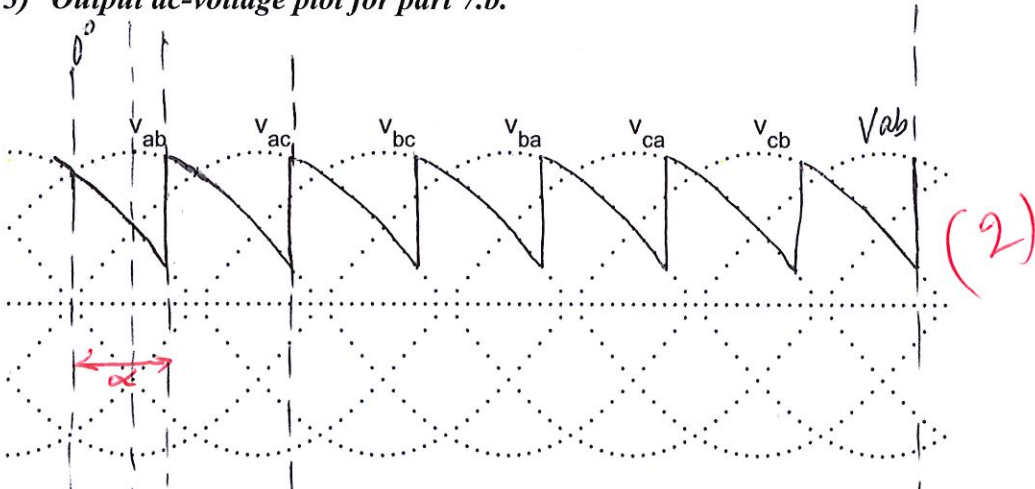

$\theta_1 = \alpha - \pi/6$   
 $\theta_1 + \pi/3 = \alpha + \pi/6$   
 $\theta_{avg} = 0 \Rightarrow V_{ab} = \sqrt{2} V_L \cos \theta \Rightarrow V_{dc} = \frac{1}{\pi/3} \int_{\alpha - \pi/6}^{\alpha + \pi/6} \sqrt{2} V_L \cos \theta \cdot d\theta = \frac{3\sqrt{2} V_L \cos \alpha}{\pi}$  (1)