

Lösningar Elektronik aug 2011

①

1a. Stor inresistans, liten utresistans.

1b. Induktans i anslutningar.

1c. Laddning, värning.

1d. $\beta = \frac{2,2k\Omega}{2,2k\Omega + 82k\Omega} = 0,0261$

1e. Gränsvfall: $U_{GS} = 4V$, $U_{DS} = 1V$

Område ?

$$U_{DS} = 1V \quad U_{GS} - V_t = 4V - 1V = 3V$$


$U_{DS} < U_{GS} - V_t \Rightarrow$ Triodområdet!

$$I_D = k \cdot \left\{ (U_{GS} - V_t) \cdot U_{DS} - \frac{1}{2} U_{DS}^2 \right\} =$$

$$= 1mA/V^2 \left\{ (4V - 1V) \cdot 1V - \frac{1}{2} \cdot (1V)^2 \right\} = \underline{2,5mA}$$


$$I_D = \frac{4V}{R} - I_L = \frac{4V}{R} - \frac{1V}{2k\Omega} = \frac{4V}{R} - 0,5mA \Rightarrow \frac{4V}{R} - 0,5mA = 2,5mA \Rightarrow$$
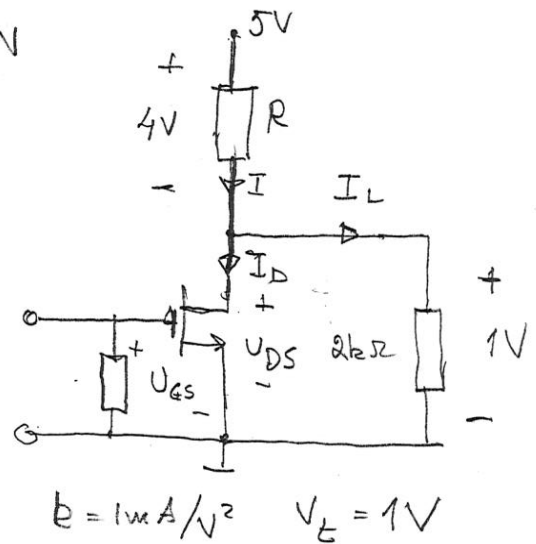
$$\Rightarrow \underline{R = 1,33k\Omega}$$



1f. $T(j\omega) = 1 \Rightarrow \frac{j\omega}{B - \omega^2 + jA\omega} = 1 \Rightarrow$
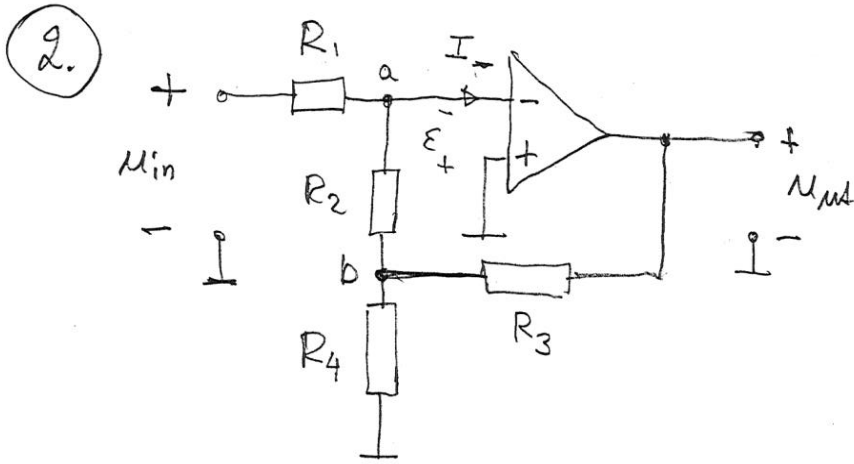
$$\underline{A=1} \quad B - \omega^2 = 0 \quad \Rightarrow B = (2\pi \cdot 5000)^2 = \underline{987 \cdot 10^6}$$



Ideal OP \Rightarrow
 $I_- = 0$
 Motkopplung \Rightarrow
 $\varepsilon = 0 \Rightarrow$
 $U_a = 0$

Nodanalyse (ströme mit)

(a)
$$\frac{0 - U_{in}}{R_1} + \frac{0 - U_b}{R_2} = 0 \Rightarrow U_b = -\frac{R_2}{R_1} \cdot U_{in} \quad (1)$$

(b)
$$\frac{U_b - 0}{R_2} + \frac{U_b}{R_4} + \frac{U_b - U_{Mut}}{R_3} \Rightarrow$$

$$\Rightarrow U_{Mut} = \left(\frac{R_3}{R_2} + \frac{R_3}{R_4} + 1 \right) \cdot U_b \quad (2). \quad (1) \text{ oder } (2) \Rightarrow$$

$$\frac{U_{Mut}}{U_{in}} = - \frac{R_2}{R_1} \cdot \left(\frac{R_3}{R_2} + \frac{R_3}{R_4} + 1 \right)$$

$$U_a = 0 \Rightarrow \underline{\underline{R_{in}} = R_1}$$

(3)

(3)

$$F(s) = \frac{72 \cdot 10^{10} \cdot s^2}{(s+120)(s+250)(s+20 \cdot 10^3)(s+200 \cdot 10^3)} =$$

$$= 72 \cdot 10^{10} \cdot \frac{s}{s+120} \cdot \frac{s}{s+250} \cdot \frac{1}{s+20 \cdot 10^3} \cdot \frac{1}{s+200 \cdot 10^3}$$

HP
HP
LP
LP

|F|_{max} : Inträffar vid mellanhöga frekvenser
 $250 \ll \omega \ll 20 \cdot 10^3$. Då gäller alltså

$$F(s) \approx 72 \cdot 10^{10} \cdot \frac{s \cdot s \cdot 1 \cdot 1}{s \cdot s \cdot 20 \cdot 10^3 \cdot 200 \cdot 10^3} = \frac{72 \cdot 10^{10}}{4 \cdot 10^9} =$$

$$= \underline{\underline{180 \text{ ggr}}} = \underline{\underline{45,1 \text{ dB}}}$$

Stigtid: Bestäms av $\omega_{01} = 20 \cdot 10^3$ och $\omega_{02} = 200 \cdot 10^3$:

$$\frac{1}{\omega_{0TOT}} \approx 1,1 \cdot \sqrt{\frac{1}{\omega_{01}^2} + \frac{1}{\omega_{02}^2}} = 1,1 \cdot \sqrt{\frac{1}{(20 \cdot 10^3)^2} + \frac{1}{(200 \cdot 10^3)^2}} \Rightarrow$$

$$\omega_{0TOT} = 18,09 \cdot 10^3 \text{ rad/s.}$$

$$t_r = \frac{2,2}{\omega_0} = \underline{\underline{0,122 \text{ ms}}}$$


Pulsfall: Bestäms av $\omega_{M1} = 120$ och $\omega_{M2} = 250$:

$$\text{Prel.} = \frac{\Delta t}{\tau_{TOT}} \cdot 100\% = \Delta t (\omega_{M1} + \omega_{M2}) \cdot 100\% =$$

$$= 0,5 \text{ ms} \cdot (120 \text{ rad/s} + 250 \text{ rad/s}) \cdot 100\% = \underline{\underline{18,5\%}}$$

④ Små signalschema:

④

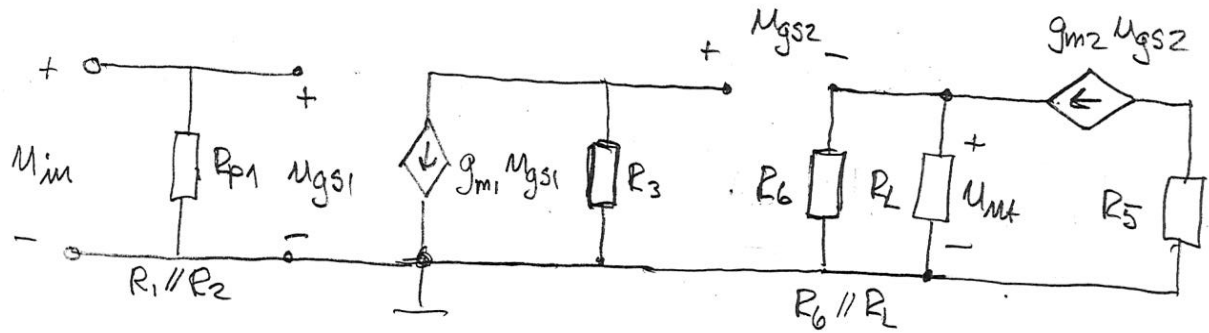

$$\frac{U_{ut}}{U_{in}} : -R_3 \cdot g_{m1} U_{gs1} = U_{gs2} + R_6 // R_L \cdot g_{m2} U_{gs2} \quad (1)$$


$$U_{gs1} = U_{in} \quad (2)$$

$$U_{ut} = g_{m2} U_{gs2} \cdot R_6 // R_L \quad (3)$$

$$(1) \text{ och } (2) \text{ ger } U_{in} = - \frac{1 + g_{m2} \cdot R_6 // R_L}{g_{m1} R_3} \cdot U_{gs2} \quad (4)$$

$$(3) \text{ och } (4) \text{ ger } \frac{U_{ut}}{U_{in}} = - g_{m1} R_3 \cdot \frac{g_{m2} \cdot R_6 // R_L}{1 + g_{m2} \cdot R_6 // R_L}$$

$$R_{ut} : R_{ut} = \frac{U_{ut}}{i_{ut}} \Big|_{U_{in}=0} \text{ utan } R_L \Rightarrow U_{gs1} = 0$$

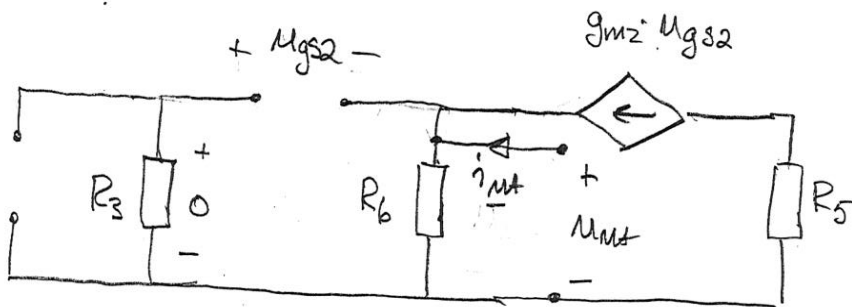


$$\left. \begin{aligned} U_{ut} &= (i_{ut} + g_{m2} U_{gs2}) \cdot R_6 \\ U_{gs2} &= -U_{ut} \end{aligned} \right\} \Rightarrow U_{ut} (1 + g_{m2} R_6) = R_6 \cdot i_{ut} \Rightarrow$$

$$R_{ut} = \frac{U_{ut}}{i_{ut}} = \frac{R_6}{1 + g_{m2} R_6}$$

5

5

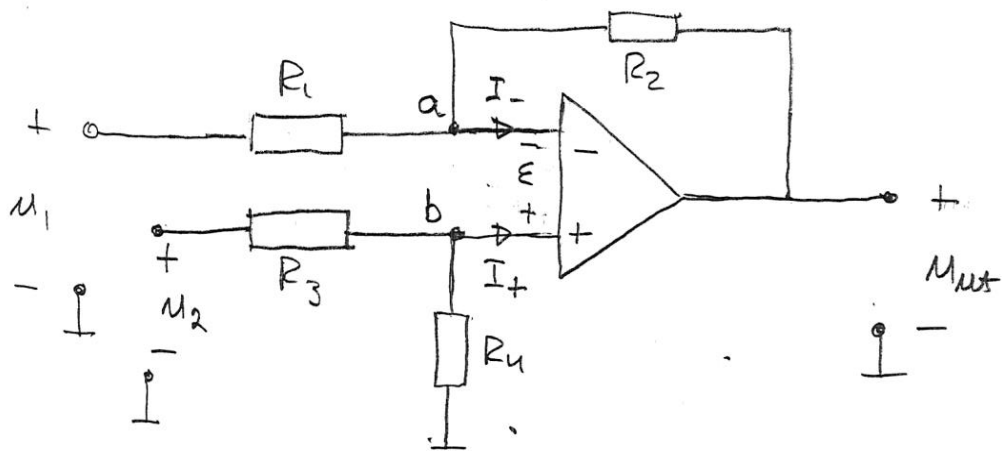

Ideal OP $\Rightarrow I_+ = I_- = 0$

Motkoppling $\Rightarrow \epsilon = 0$, så att $V_a = V_b$.

$R_1 = 1,1 \text{ k}\Omega$ $R_2 = 99 \text{ k}\Omega$ $R_3 = 99 \text{ k}\Omega$ $R_4 = 101 \text{ k}\Omega$

Bestäm först u_{Mut} som funktion av u_1 och u_2 :

Nodanalys (strömmar ut):

a $\frac{V_a - u_1}{R_1} + \frac{V_a - u_{Mut}}{R_2} = 0$ (1)

b $\frac{V_b - u_2}{R_3} + \frac{V_b}{R_4} = 0$ (2)

$V_a = V_b$ (3)

(2) ger $\left(\frac{1}{R_3} + \frac{1}{R_4}\right) \cdot V_b = \frac{u_2}{R_3} \Rightarrow V_b = \frac{R_4}{R_3 + R_4} \cdot u_2$ (4)

(1) ger $V_a \cdot \left(\frac{1}{R_1} + \frac{1}{R_2}\right) = \frac{u_1}{R_1} + \frac{u_{Mut}}{R_2} \Rightarrow$

$V_a = \frac{R_1 R_2}{R_1 + R_2} \cdot \frac{u_1}{R_1} + \frac{R_1 R_2}{R_1 + R_2} \cdot \frac{u_{Mut}}{R_2} = \frac{R_2}{R_1 + R_2} \cdot u_1 + \frac{R_1}{R_1 + R_2} \cdot u_{Mut}$ (5)

(3) ger $\frac{R_4}{R_3 + R_4} \cdot u_2 = \frac{R_2}{R_1 + R_2} \cdot u_1 + \frac{R_1}{R_1 + R_2} \cdot u_{Mut} \Rightarrow$

$u_{Mut} = \frac{R_1 + R_2}{R_1} \cdot \left(\frac{R_4}{R_3 + R_4} \cdot u_2 - \frac{R_2}{R_1 + R_2} \cdot u_1 \right)$ (6)

DM-förstärkning: $u_2 = \frac{u_{DM}}{2}$, $u_1 = -\frac{u_{DM}}{2} \Rightarrow$ (6)

$$u_{MutDM} = \frac{R_1 + R_2}{R_1} \left(\frac{R_4}{R_3 + R_4} + \frac{R_2}{R_1 + R_2} \right) \cdot \frac{u_{DM}}{2} =$$

$$= \frac{100,1}{1,1} \cdot \left(\frac{101}{101,9} + \frac{99}{109,1} \right) \cdot \frac{u_{DM}}{2} = 90,098 u_{DM} \Rightarrow$$

$$A_{DM} = \frac{u_{MutDM}}{u_{DM}} = \underline{\underline{90,098 \text{ ggr}}}$$


CM-förstärkning: $u_1 = u_2 = u_{CM} \Rightarrow$

$$u_{MutCM} = \frac{R_1 + R_2}{R_1} \left(\frac{R_4}{R_3 + R_4} - \frac{R_2}{R_1 + R_2} \right) \cdot u_{CM} = 0,19627 \cdot u_{CM}$$

$$\Rightarrow A_{CM} = \frac{u_{MutCM}}{u_{CM}} = \underline{\underline{0,19627 \text{ ggr}}}$$


$$CMRR = \left| \frac{A_{DM}}{A_{CM}} \right| = \frac{90,098}{0,19627} = \underline{\underline{459 \text{ ggr}}} = \underline{\underline{53,2 \text{ dB}}}$$

6. Småsignal schema

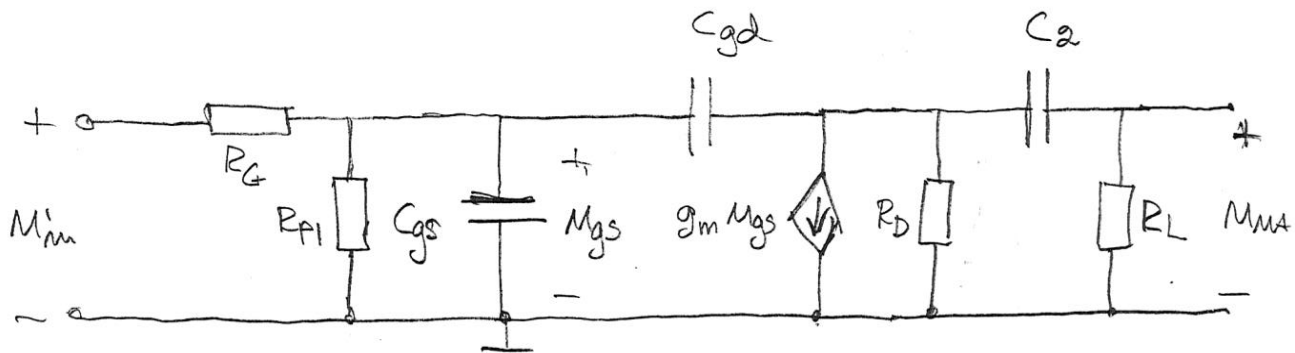

$R_G = 500 \Omega$ $R_{P1} = R_1 // R_2 = 200 k\Omega$ $R_D = 4 k\Omega$ $R_L = 5 k\Omega$
 $C_2 = 250 nF$ $g_m = 50 mA/V$ $C_{gs} = 30 pF$ $C_{gd} = 3 pF$ $r_o = \infty$

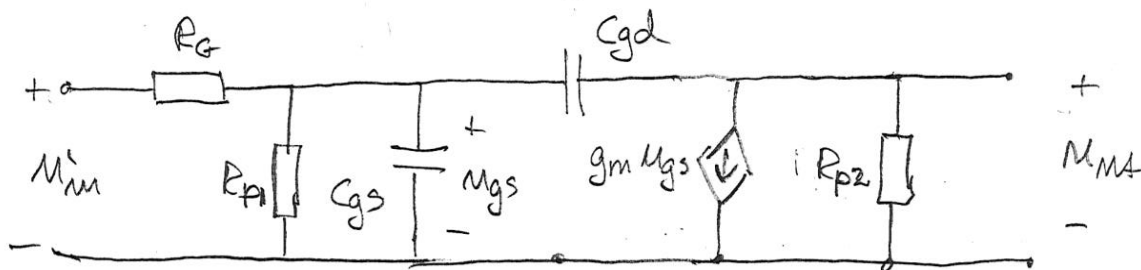Höga frekvenser: $\frac{1}{\omega C_2} \approx 0$ $R_{P2} = R_D // R_L = 2,22 k\Omega$




C_{gd} delas upp med Millers sats:

$C_{M1} = (1 - k) \cdot C_{gd}$ $C_{M2} = (1 - \frac{1}{k}) \cdot C_{gd}$, där

$k \approx \frac{U_{ut}}{U_{gs}} = \frac{-R_{P2} \cdot g_m U_{gs}}{U_{gs}} = -R_{P2} \cdot g_m = -2,22 k\Omega \cdot 50 mA/V = -111$

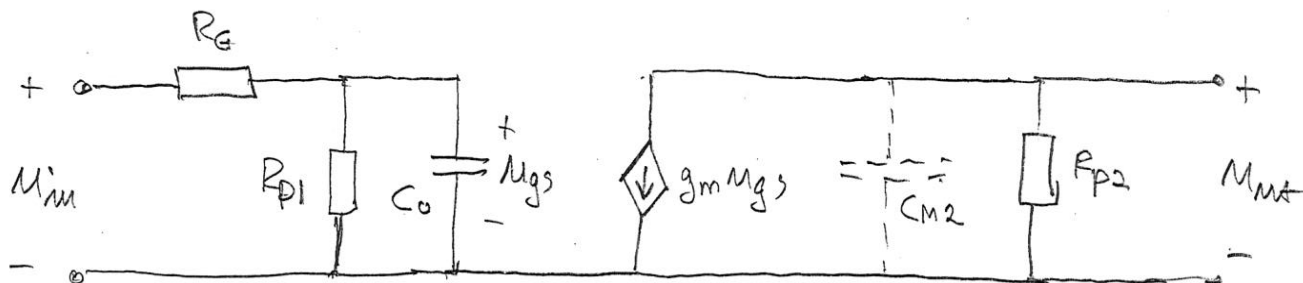$\Rightarrow C_{M1} = 112 \cdot 3 pF = 336 pF$ $C_{M2} \approx 1,01 \cdot 3 pF = 3,03 pF$ (försummas)



$C_0 = C_{gs} + C_{M1} = 30 pF + 336 pF = 366 pF$

$$R_{p1} \gg R_G \Rightarrow$$

$$M_{gs} \approx \frac{\frac{1}{sC_0}}{\frac{1}{sC_0} + R_G} \cdot U_{in} = \frac{1}{1 + sR_G C_0} \cdot U_{in}$$


$$U_{out} = -R_{p2} \cdot g_m M_{gs} = -\frac{g_m R_{p2}}{1 + sR_G C_0} \cdot U_{in} \Rightarrow$$

$$\frac{U_{out}}{U_{in}} = -\frac{g_m R_{p2}}{1 + sR_G C_0}$$

Den övre gränsvinkel frekvensen blir då

$$\omega_0 = \frac{1}{R_G C_0} = \frac{1}{500 \Omega \cdot 366 \text{ pF}} = 5,46 \text{ Mrad/s} \Rightarrow \underline{\underline{f_0 = 870 \text{ kHz}}}$$

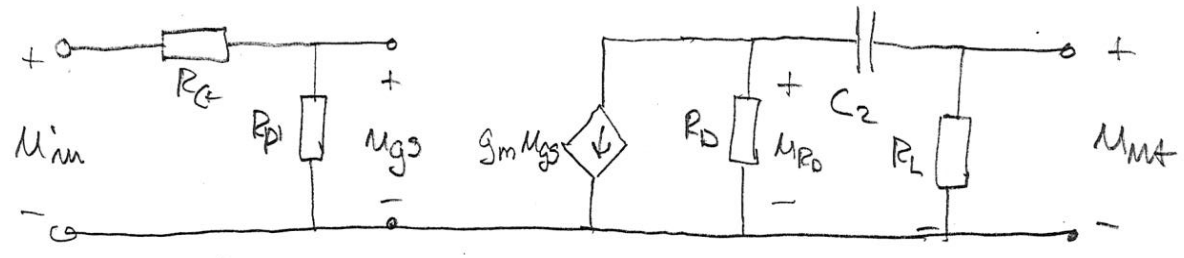Låga frekvenser: $\frac{1}{\omega C_{gs}} \approx \infty$, $\frac{1}{\omega C_{gd}} \approx \infty$, $\frac{1}{\omega C_2} \gg 0$



$$M_{gs} = \frac{R_{p1}}{R_{p1} + R_G} \cdot U_{in} = 0,9975 \cdot U_{in} \approx U_{in}$$

$$\begin{aligned} U_{out} &= \frac{R_L}{R_L + \frac{1}{sC_2}} \cdot U_{pD} = \frac{sR_L C_2}{1 + sR_L C_2} \cdot U_{pD} = \\ &= \frac{sR_L C_2}{1 + sR_L C_2} \left(-g_m U_{gs} \cdot R_D \parallel \left(R_L + \frac{1}{sC_2} \right) \right) = -\frac{g_m U_{gs} \cdot sR_L C_2}{1 + sR_L C_2} \cdot \frac{R_D \cdot \left(R_L + \frac{1}{sC_2} \right)}{R_D + R_L + \frac{1}{sC_2}} = \\ &= -\frac{g_m U_{gs} \cdot sR_L C_2 \cdot R_D \cdot \left(1 + sR_L C_2 \right)}{\left(1 + sR_L C_2 \right) \cdot \left(1 + s \left(R_L + R_D \right) C_2 \right)} \quad (\text{HP}) \Rightarrow \end{aligned}$$

$$\omega_M = \frac{1}{(R_D + R_L) C_2} = 444 \text{ rad/s} \Rightarrow \underline{\underline{f_M = 70,7 \text{ Hz}}}$$