


1c

$$H(s) = \frac{10^5}{1 + \frac{s}{25}} = \frac{H_0}{1 + \frac{s}{\omega_1}}$$

$$\begin{cases} H_0 = 10^5 \\ \omega_1 = 25 \end{cases}$$

$$R_1 = 1 \text{ k}\Omega$$

$$R_2 = 99 \text{ k}\Omega$$

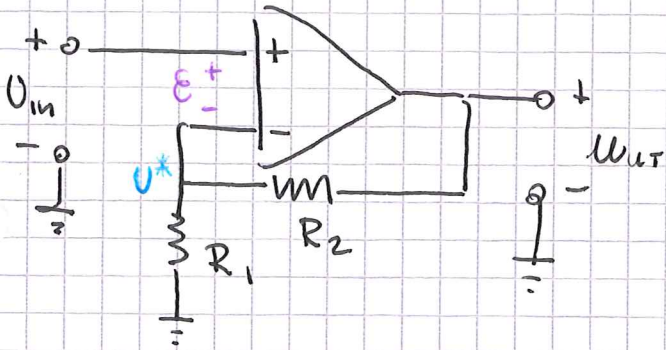

$$U^* = U_{UT} \frac{R_1}{R_1 + R_2} \quad (\text{I})$$

$$U_{in} = U^* + \varepsilon \quad (\text{II})$$

$$H(s) \varepsilon = U_{UT} \quad (\text{III})$$

(I & II & III)

$$\begin{aligned} U_{in} &= U_{UT} \frac{R_1}{R_1 + R_2} + \frac{U_{UT}}{H(s)} = \\ &= U_{UT} \left(\frac{1}{H(s)} + \frac{R_1}{R_1 + R_2} \right) \end{aligned}$$

$$3) \quad \frac{U_{UT}}{U_{in}} = \frac{H(s) (R_1 + R_2)}{R_1 + R_2 + R_1 H(s)} = \frac{H(s)}{1 + \frac{R_1}{R_1 + R_2} H(s)} = \frac{H(s)}{1 + \beta H(s)}$$

$$\beta = \frac{1}{1 + 99} = \frac{1}{100}$$

now substitute $H(s) = \frac{H_0}{1 + s/\omega_1}$

$$= \frac{H_0}{1 + s/\omega_1} \cdot \frac{1}{1 + \beta \frac{H_0}{1 + s/\omega_1}} = \frac{H_0}{1 + \frac{s}{\omega_1} + \beta H_0}$$

$$= \frac{H_0}{1 + \beta H_0 + \frac{s}{\omega_1}} \cdot \frac{1}{1 + \beta H_0} = \frac{H_0}{1 + \beta H_0} \cdot \frac{1}{\omega_1 (1 + \beta H_0)}$$



$\rightarrow H_{MAX} \approx \frac{1}{\beta} = 100 \text{ 99}$
(because H_0 is big)

$$\omega_{s \text{ tot}} = \omega_1 (1 + \beta H_0)$$

25 rad/sec

1e

offset spennings

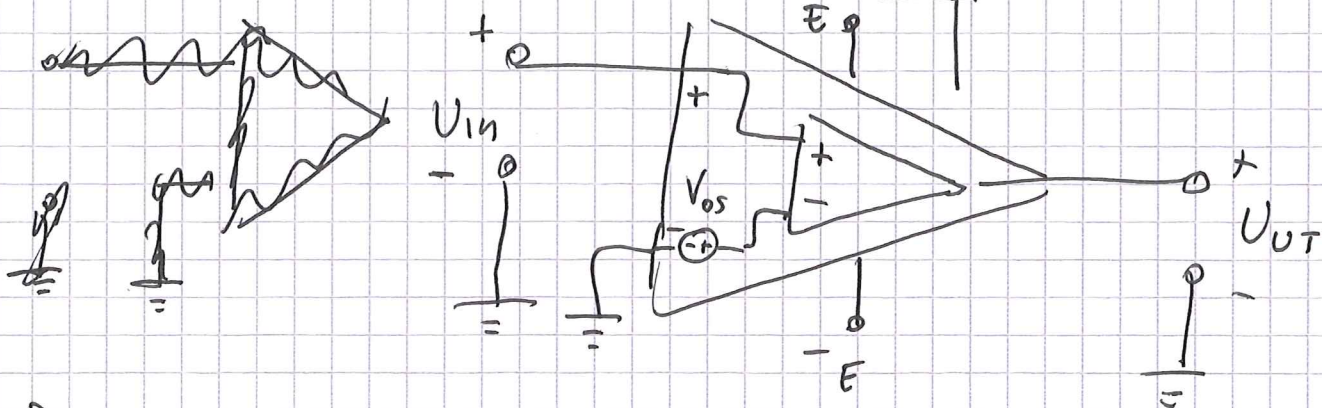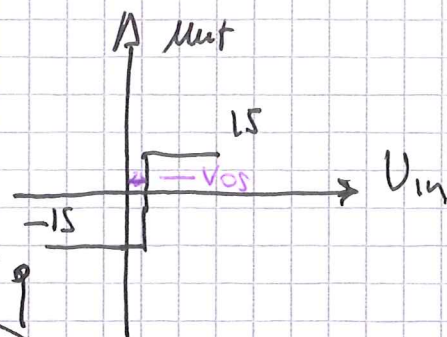

1f

$$H(s) = \frac{a}{2s^2 + 16bs + 10}$$

Real Poles

$$2s^2 + 16bs + 10$$

$$s^2 + 8bs + 5$$

we need to find solutions of this and make sure they are real

$$s_{1,2} = \frac{-8b \pm \sqrt{8^2 b^2 - 4 \cdot 5}}{2}$$

$$= \frac{-8b \pm \sqrt{16b^2 - 5}}{2}$$


$$16b^2 - 5 \geq 0$$

$$b^2 \geq \frac{5}{16}$$

$$b > \frac{\sqrt{5}}{4}$$

$$b < -\frac{\sqrt{5}}{4}$$

1d

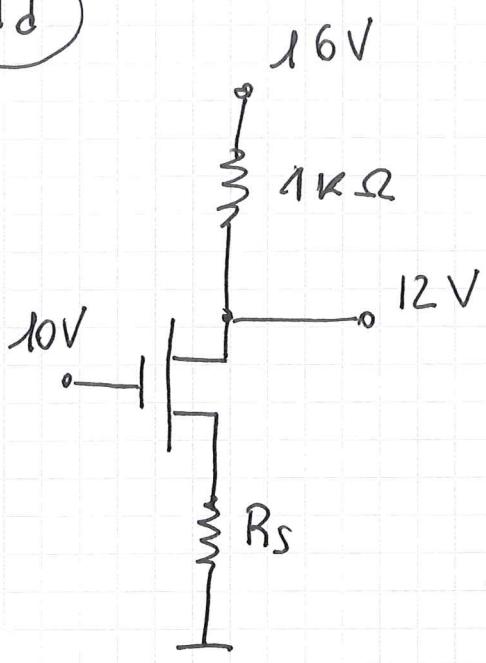

$$R_S = ?$$

$$V_D = 12V$$

$$V_G = 10V$$

$$V_t = 3V$$

$$k = 4 \text{ mA/V}^2$$

$$I_D = \frac{16 - 12 \text{ V}}{1 \text{ k}\Omega} = 4 \text{ mA}$$

$$V_S = I_D R_S$$

$$V_{DS} : V_{GS} - V_t$$

$$I_D = (V_{GS} - V_t)^2 \frac{k}{2} \Rightarrow V_{GS} = \pm \sqrt{\frac{2 I_D}{k}} + V_t$$

$$V_D - V_S : V_G - V_S - V_t$$

$$= \pm \sqrt{2} + 3 = 4.4 \text{ V}$$

$$\begin{cases} 12 - V_S : 10 - V_S - 3 \\ V_S > 0 \text{ \& \ } V_S < 12 \end{cases}$$

$$12 - V_S : 7 - V_S$$

always >

So we are in saturation area


MA NON SAT

$$V_{GS} = V_G - V_S \Rightarrow V_S = V_G - V_{GS}$$

$$R_S = \frac{V_S}{I_D} = \frac{V_G - V_{GS}}{I_D}$$

$$\Rightarrow R_S = \frac{10 - 4.4 \text{ V}}{4 \text{ mA}} = 1.4 \text{ k}\Omega$$

2

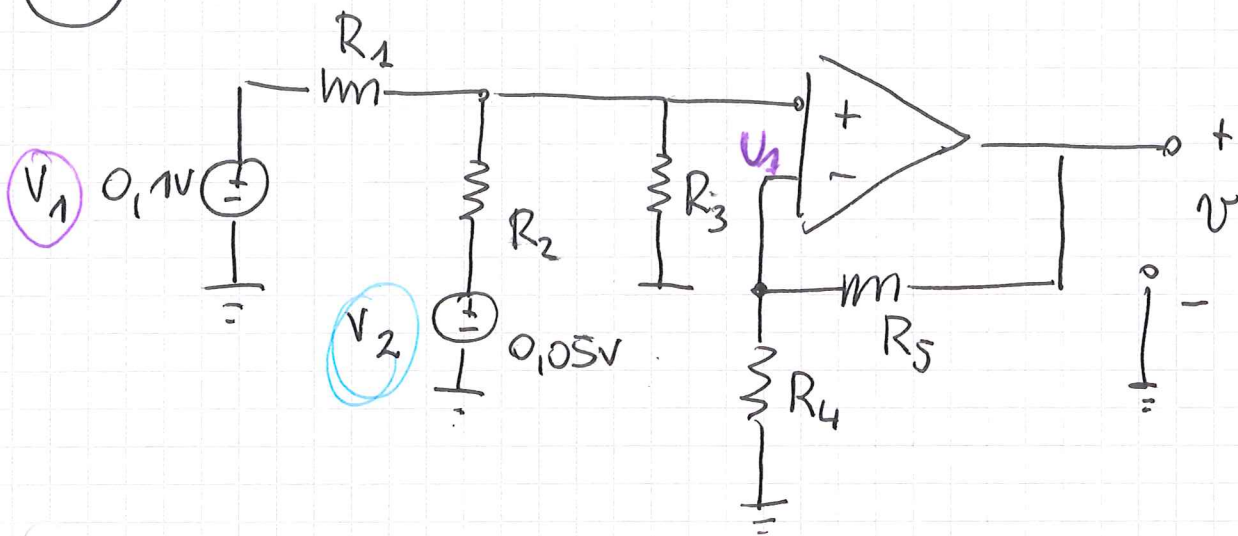

$R_1 = 1k\Omega, R_2 = 2k\Omega, R_3 = 2k\Omega, R_4 = 1k\Omega, R_5 = 3k\Omega$

Principle

Superposition of effects

$$R_2 // R_3 = \frac{1}{\frac{1}{R_2} + \frac{1}{R_3}} = \frac{R_2 R_3}{R_2 + R_3}$$

$$R_{eq} = \frac{R_2 R_3}{R_3 + R_2}$$

$$U = U_1 \left(1 + \frac{R_5}{R_4} \right) = U_1 \frac{R_4 + R_5}{R_4}$$

$= 0,0625 \cdot \frac{4}{1} = 0,25V$

$U_1 = U_2 + U_3$

$U_2 = V_1 \frac{R_2 // R_3}{R_1 + R_2 // R_3} \Big|_{V_2=0} = V_1 \frac{R_2 R_3}{R_3 + R_2} \frac{1}{R_1 + \frac{R_2 R_3}{R_3 + R_2}}$


$U_3 = V_2 \frac{R_1 // R_3}{R_2 + R_1 // R_3} \Big|_{V_1=0} = V_2 \frac{R_1 R_3}{R_3 + R_1} \frac{1}{R_2 + \frac{R_1 R_3}{R_3 + R_1}}$

$U_2 = V_1 \frac{R_2 R_3}{R_1(R_3 + R_2) + R_2 R_3} = 0,1 \frac{4}{4 + 4} = 0,05V$

$U_3 = V_2 \frac{R_1 R_3}{R_2(R_3 + R_1) + R_1 R_3} = 0,05 \frac{2}{6 + 2} = 0,0125V$

$U = 0,0625$

3

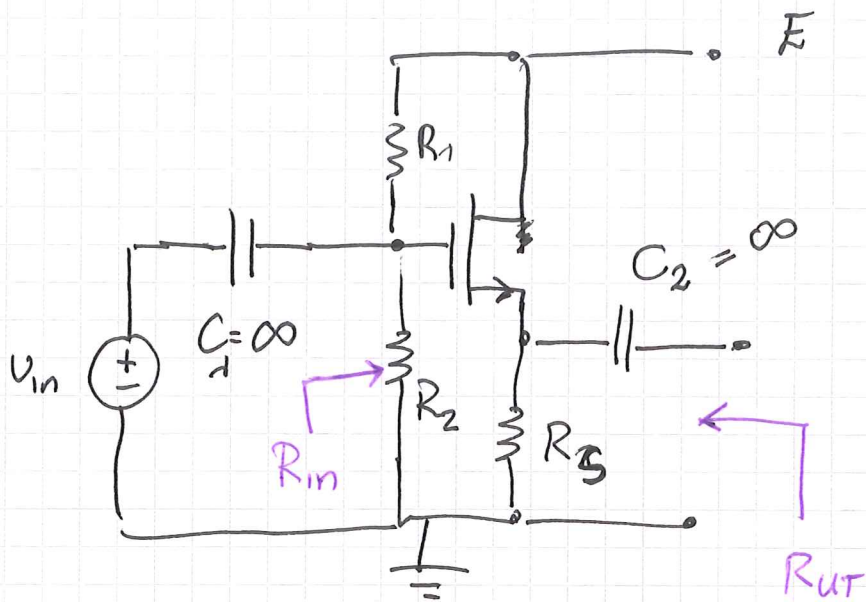

$$V_t = 1V$$

$$k = 2mA/V^2$$

$$R_1 = 100k\Omega$$

$$R_2 = 220k\Omega$$

$$R_S = 2k\Omega$$


$$E = 16V$$

$$I_D = 4mA$$

$$\left[R_{in}, R_{out}, \frac{U_{ur}}{U_{in}} \right]$$

$$g_m = \sqrt{2k I_D} = \sqrt{2 \cdot 2 \cdot 4 \frac{mA \cdot mA}{V^2}} = \frac{4mA}{V}$$

small signals model

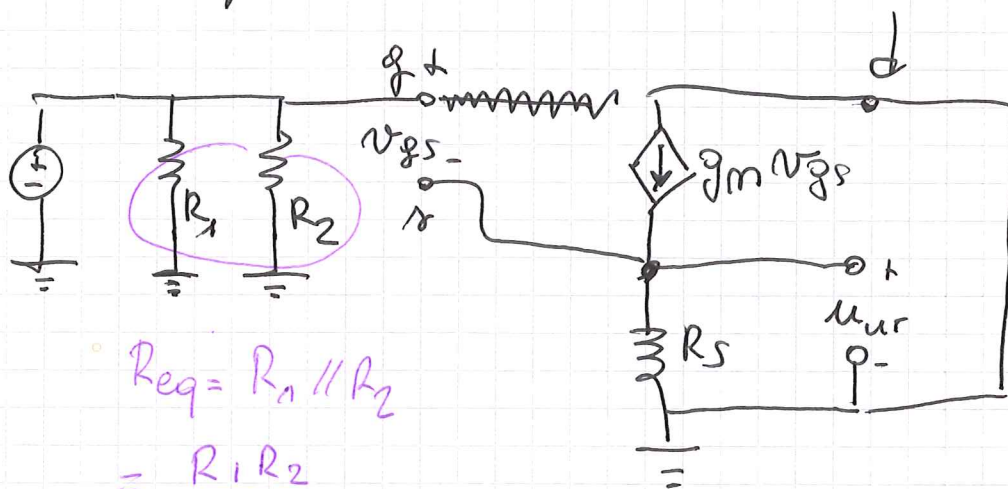

$$R_{eq} = R_1 \parallel R_2$$

$$= \frac{R_1 R_2}{R_1 + R_2}$$

$$v_s = u_{ur}$$

$$v_s = g_m v_{gs} R_S$$

$$v_g = u_{in}$$

$$v_{gs} = v_g - v_s = u_{in} - g_m v_{gs} R_S$$

$$v_{gs} (1 + g_m R_S) = u_{in}$$

$$\frac{u_{ur}}{v_{in}} = \frac{g_m R_S v_{gs}}{1 + g_m R_S v_{gs}} = \frac{g_m R_S}{1 + g_m R_S} = \frac{\frac{4mA}{V} \cdot 2k\Omega}{1 + \frac{4mA}{V} \cdot 2k\Omega} = \frac{8}{9} = 0,89$$

continua 3

$$R_{in} = \frac{U_{in}}{I_{in}} \Big|_{u_{ut}=0} = R_1 // R_2 = 68,75 \text{ k}\Omega$$

no current in R_s : does not contrib. to R_{in}

$$R_{ut} = \frac{U_{ut}}{I_{ut}} \Big|_{U_{in}=0}$$

~~$U_{ut} = \dots$~~

~~$U_{ut} = \dots$~~ $(g_m v_{gs} + i_{ut}) R_s = v_{ut}$ II

but $v_{ut} = v_s = -v_{gs}$ I


$$v_{gs} = v_g - v_s = 0 - v_s$$

I & II $\Rightarrow v_{ut} = (i_{ut} - g_m v_{ut}) R_s$

$$v_{ut} (1 + g_m R_s) = i_{ut} R_s$$

$$R_{ut} = \frac{U_{ut}}{I_{ut}} = \frac{R_s}{1 + g_m R_s} = \frac{2 \text{ k}\Omega}{1 + \frac{4 \text{ mA}}{V} \cdot 2 \text{ k}\Omega} = 222 \Omega$$

④ OSCILLATOR

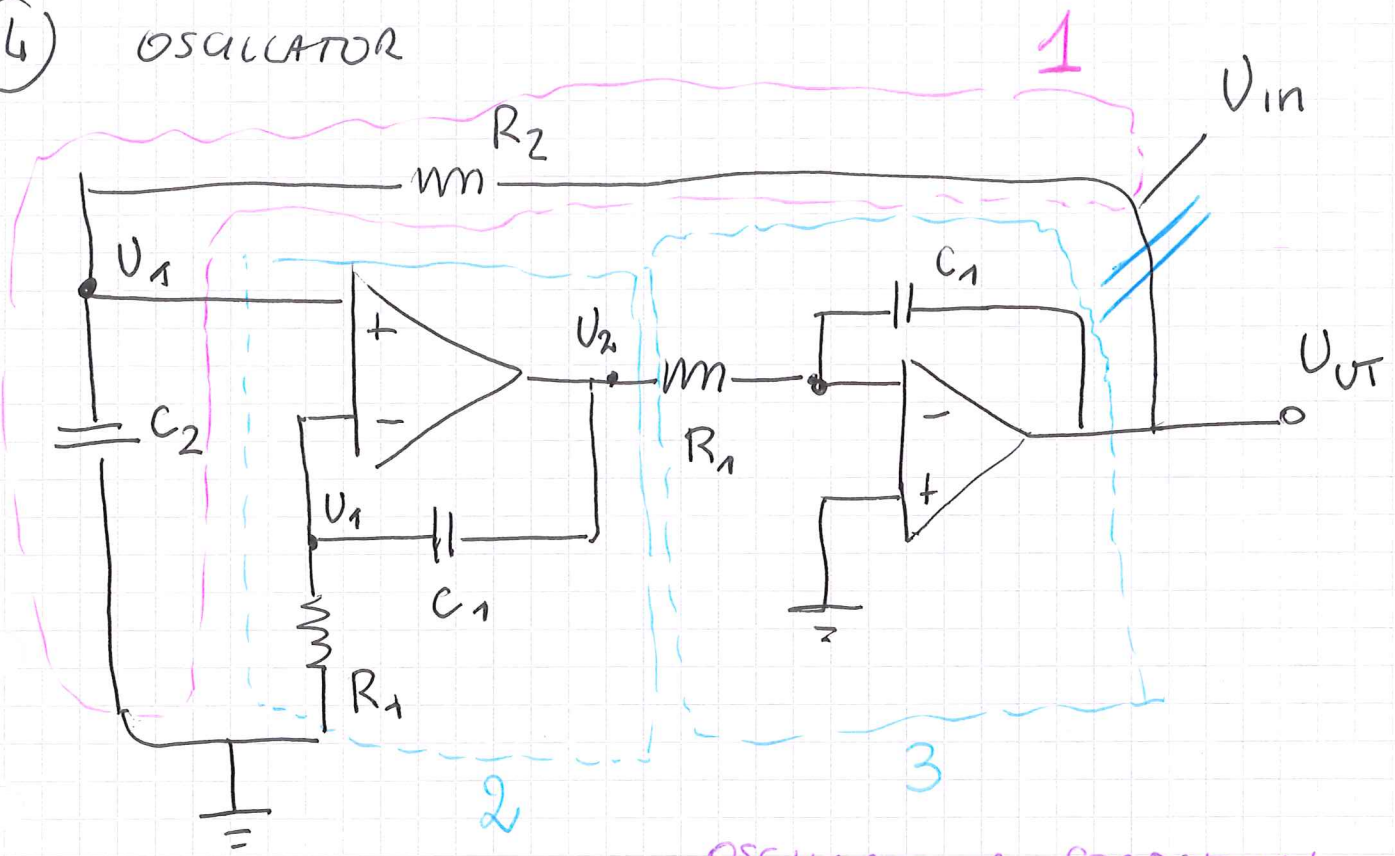

OSCILLATING CONDITION

$$T(j\omega) \equiv 1$$

$$1) U_1 = \frac{U_{in}}{\frac{1}{sC_2} + R_2} \cdot \frac{1}{sC_2} = U_{in} \frac{1}{R_2 C_2 s + 1}$$

$$2) U_2 = 1 + \frac{1}{sC_1 R_1} U_1 = \frac{R_1 s C_1 + 1}{R_1 s C_1}$$

$$3) U_{OT} = - \frac{U_2}{R_1} \frac{1}{sC_2}$$

$$(1), (2) \text{ and } (3) \quad T(s) = \frac{U_{OT}}{U_{in}} = - \frac{1}{R_2 C_2 s + 1} \frac{R_1 C_1 s + 1}{R_1 C_1 s} \frac{1}{R_1 C_1 s}$$


$$T(j\omega) = - \frac{R_1 C_1 j\omega + 1}{R_1^2 C_1^2 (j\omega)^2 (R_2 C_2 j\omega + 1)} \equiv 1$$

$$\bullet R_1 C_1 j\omega + 1 = R_2 C_2 j\omega + 1 \Rightarrow R_1 C_1 = R_2 C_2$$

$$\bullet \omega^2 R_1^2 C_1^2 = 1 \quad \omega = \sqrt{\frac{1}{R_1^2 C_1^2}} = 0,03 \cdot 10^6 \text{ rad/sec} \quad C_1 = \frac{R_2 C_2}{R_1} = \frac{4,02}{1} \text{ nF}$$

\$f = 4,83 \text{ kHz}\$

5

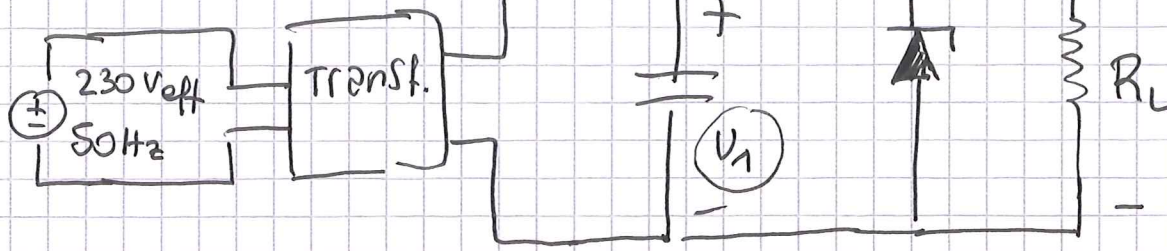


$R = 60 \Omega$

$R_L = 120 \Omega$

$E_Z = 20V$

$P_{ZMAX} = 2W$

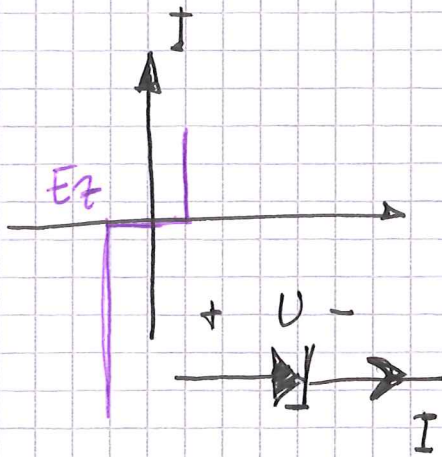

within which limits of (U_1) do we find if found

if the stabilization is maintained without

the power lost by Zener exceeds P_{ZMAX} ?

U_{1MAX} ? U_{1MIN} ?

U_{1MAX} : $P_{ZMAX} = I_{ZMAX} E_Z \Rightarrow I_{ZMAX} = \frac{P_{ZMAX}}{E_Z} = \frac{2W}{20} = 0,1A$


$U_{1MAX} = (I_{ZMAX} + I_L) R + E_Z = 16 + 20V = 36V$

$I_L = \frac{E_Z}{R_L} = \frac{20V}{120 \Omega} = 0,167A$

U_{1min} : $I_Z = 0$

$U_{1min} = I_L R + E_Z = 10 + 20 = 30V$

6

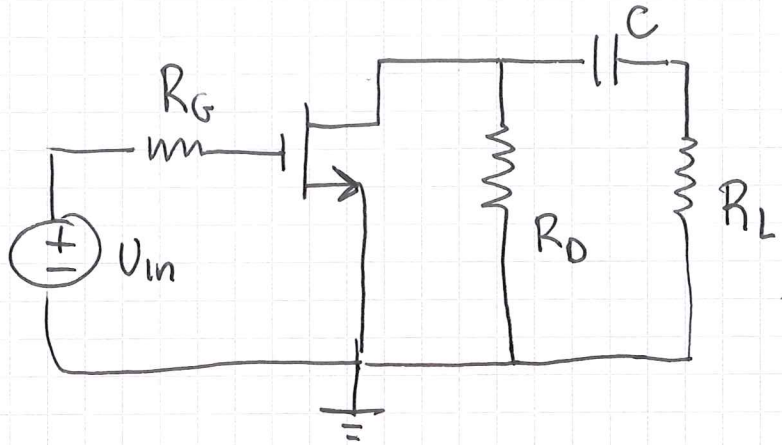


$g_m = 40 \text{ mA/V}$
 $C_{gs} = 30 \text{ pF}$
 $C_{gd} = 4 \text{ pF}$


$C = \infty \rightarrow \text{short}$ $C = 0$ (open - AUBROTT)

Bode diagram $\frac{U_{ur}}{U_{in}}$

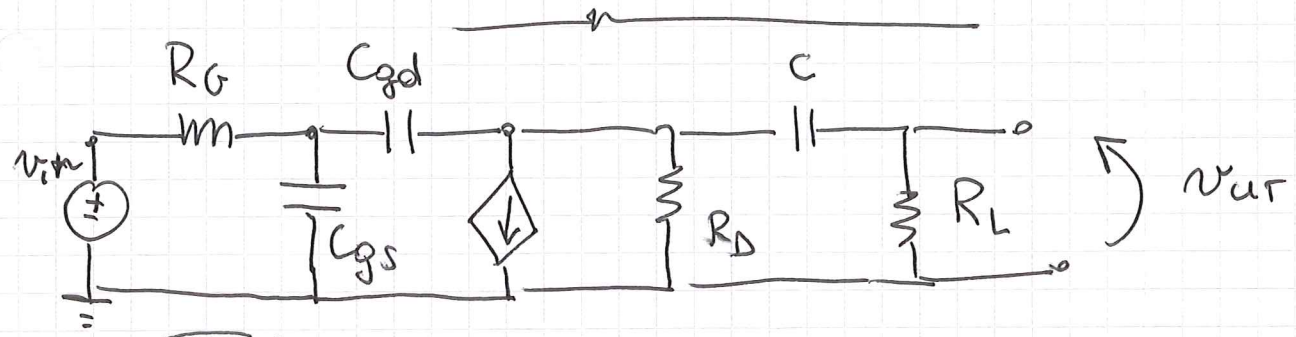$R_G = 800 \Omega$
 $R_D = 4 \text{ k}\Omega$
 $R_L = 4 \text{ k}\Omega$
 $C = 200 \text{ nF}$



Miller

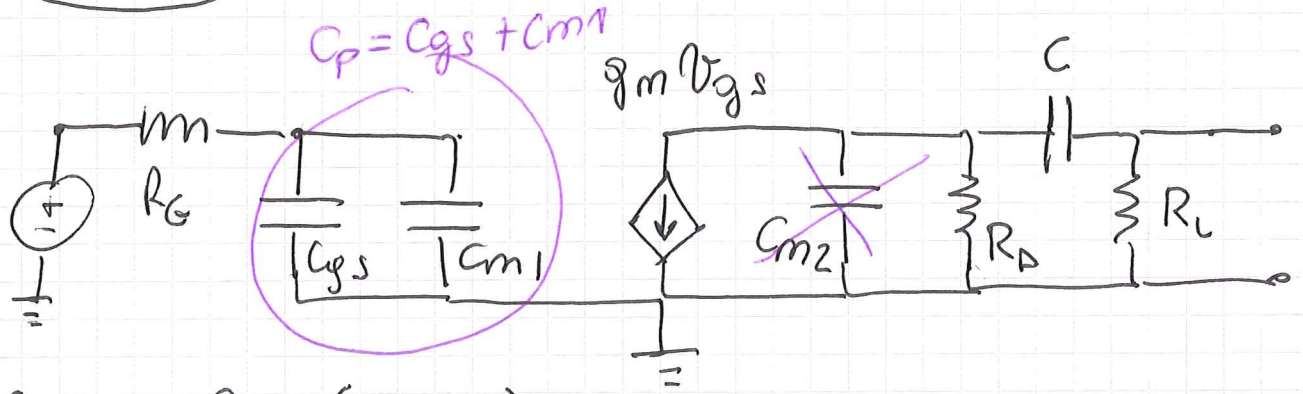


$C_{m1} = C_{gd} (1 - k)$

~~$C_{m2} = C_{gd} \frac{(k-1)}{k}$~~

$k = \frac{U_{ds}}{U_{gs}}$

6 continue

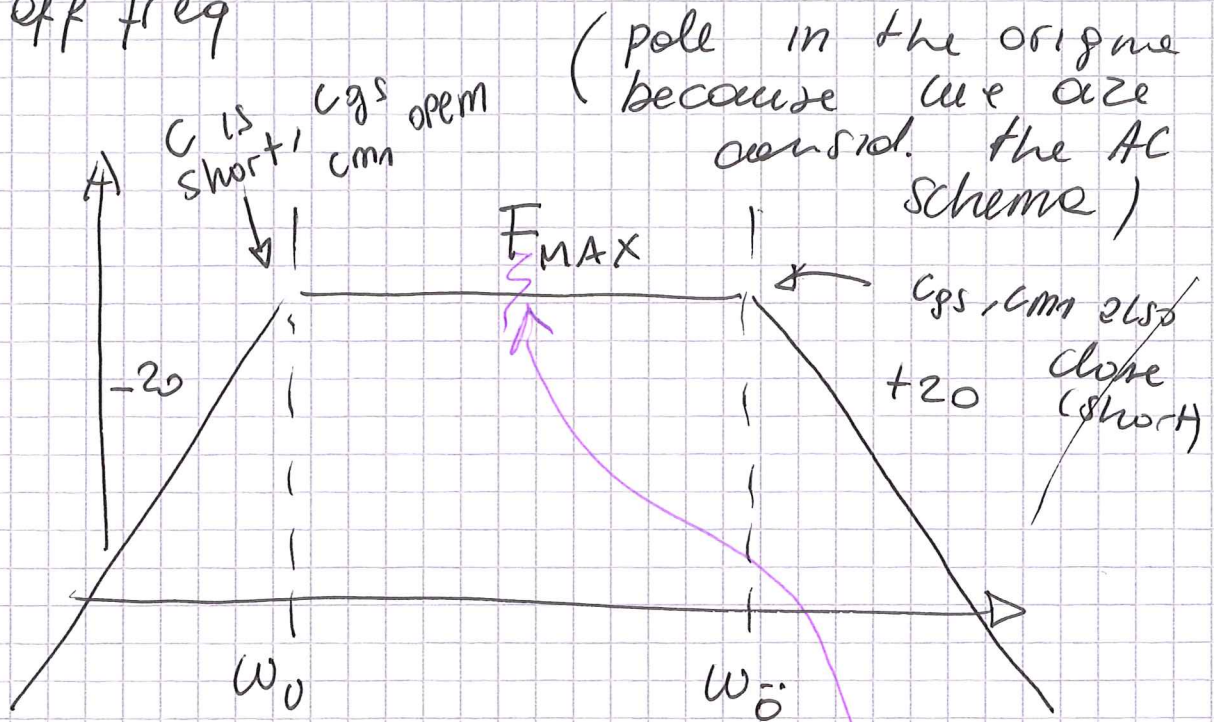The smaller capacitors are the ones that will come into play later (in freq) while the bigger will have a smaller cut off freq




F_{MAX} we need to be here

it means that C_{gs} is short and C_{mm}, C_{gs} open
 $C = \infty$ $C_{gs} = C_{mm} = 0$

$$U_{in} = v_{gs}$$
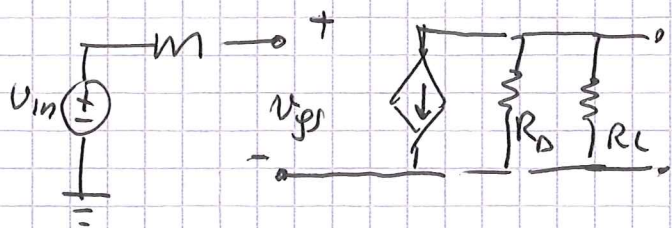
$$U_{ur} = -g_m v_{gs} \cdot R_D // R_L$$



$$\frac{U_{ur}}{U_{in}} = -g_m R_D // R_L$$

current divider


ω_0 now we need to express transfer function but still C_{gs} and $C_{mm} = 0$

$$U_{ur} = -g_m v_{gs} \frac{R_D}{R_D + \frac{1}{sC} + R_L} \cdot R_L = -g_m v_{gs} \frac{R_D R_L sC}{1 + sC(R_D + R_L)}$$

$$U_{in} = v_{gs} \Rightarrow \omega_u = \frac{1}{C(R_D + R_L)}$$

Q continue

now we want to find $\omega_{\ddot{o}}$

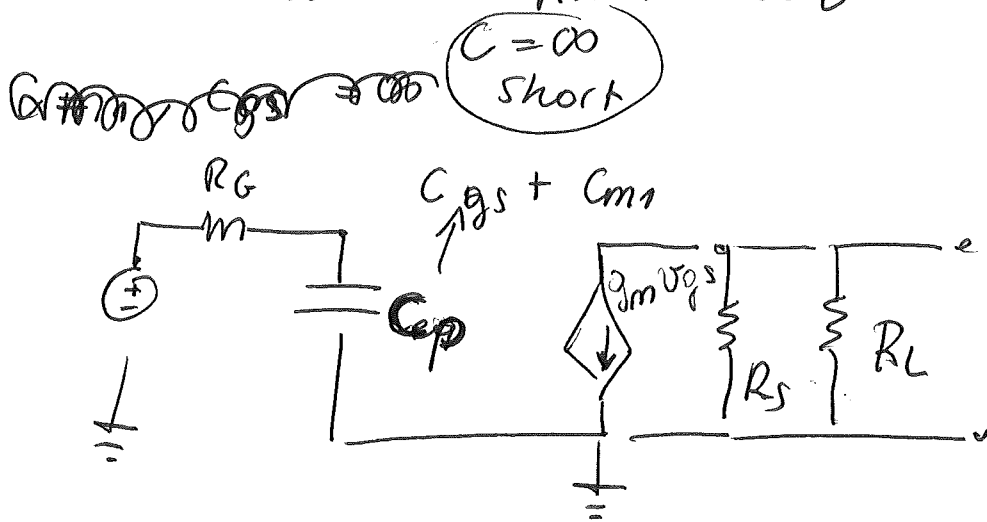

$$v_{gs} = \frac{1}{sC_p} \frac{1}{R_G + \frac{1}{sC_p}} U_{in} \quad U_{in} = v_{gs} sC_p \left(R_G + \frac{1}{sC_p} \right)$$

$$U_{out} = -g_m v_{gs} R_S \parallel R_L$$

$$\frac{U_{out}}{U_{in}} = \frac{-g_m v_{gs} R_S \parallel R_L}{v_{gs} sC_p \left(R_G + \frac{1}{sC_p} \right)} = \frac{-g_m R_S \parallel R_L}{sC_p R_G + 1}$$

$$\omega_{\ddot{o}} = \frac{1}{C_p R_G} = \frac{1}{(C_{gs} + C_{mi}) R_G}$$

CURRENT DIVIDER